

**Circuits
from the Lab™**
Reference Circuits

Circuits from the Lab™ reference circuits are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit www.analog.com/CN0241.

Devices Connected/Referenced

ADA4096-2	30 V, Micropower, Overvoltage Protection, Rail-to-Rail Input/Output Amplifier
AD7920	250 kSPS, 12-bit, 250 kSPS ADC in 6-Lead SC70
ADP3336	High Accuracy Ultralow I_{Q} 500 mA anyCAP® Adjustable Low Dropout Linear Regulator

High-Side Current Sensing with Input Overvoltage Protection

EVALUATION AND DESIGN SUPPORT

Circuit Evaluation Boards

[CN-0241 Circuit Evaluation Board \(EVAL-CN0241-SDPZ\)](#)
[System Demonstration Platform \(EVAL-SDP-CB1Z\)](#)

Design and Integration Files


[Schematics, Layout Files, Bill of Materials](#)

CIRCUIT FUNCTION AND BENEFITS

High-side current monitors are likely to encounter overvoltage conditions from transients or when the monitoring circuits are connected, disconnected, or powered down. This circuit, shown

in Figure 1, uses the overvoltage protected [ADA4096-2](#) op amp connected as a difference amplifier to monitor the high-side current. The [ADA4096-2](#) has input overvoltage protection, without phase reversal or latch-up, for voltages of 32 V higher than and lower than the supply rails.

The circuit is powered by the [ADP3336](#) adjustable low dropout 500 mA linear regulator, which can also be used to supply power to other parts of the system, if desired. Its input voltage can range from 5.2 V to 12 V when set for a 5 V output. To save power, the current sensing circuit can be powered down by removing power to the [ADP3336](#); however, the power source, such as a solar panel, can still operate.

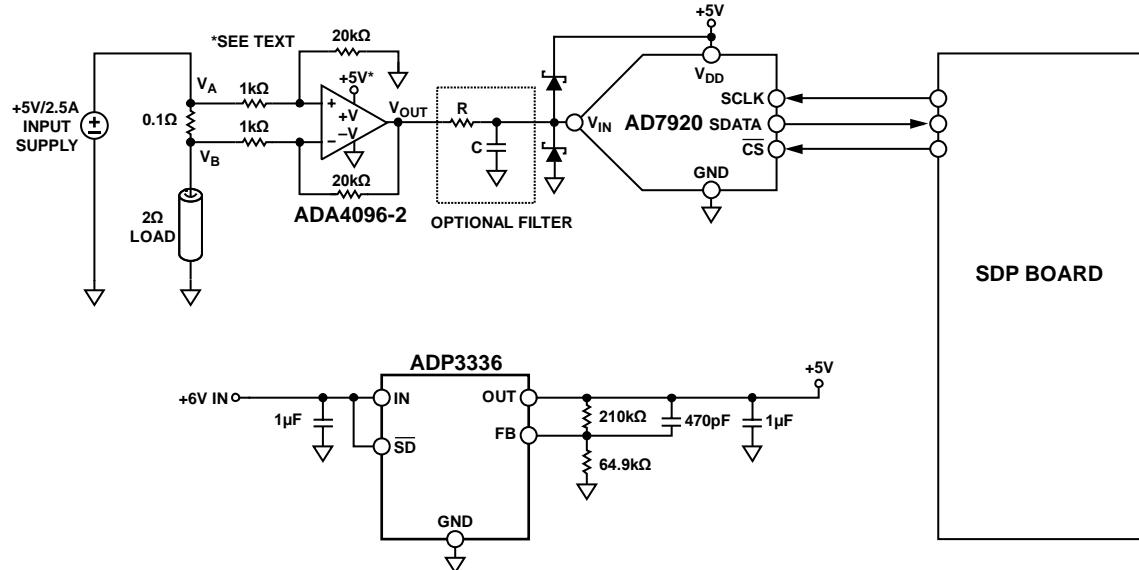

10154901

Figure 1. High-Side Current Sensing with Input Overvoltage Protection (Simplified Schematic: All Connections and Decoupling Not Shown)

Rev. A

Circuits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

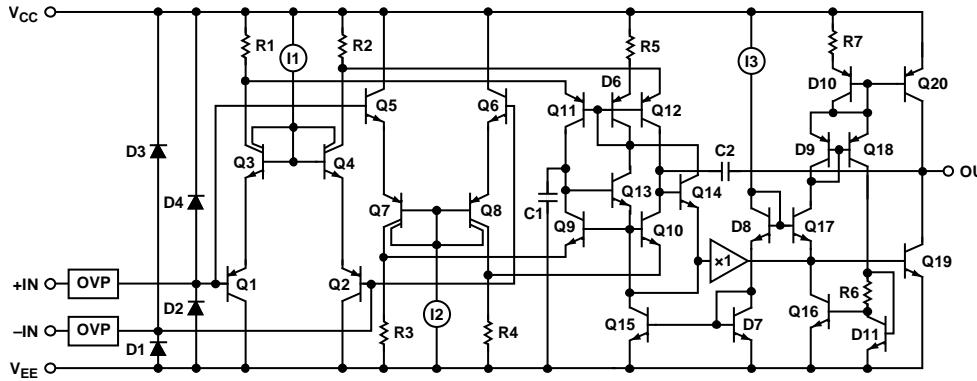


Figure 2. ADA4096-2 Simplified Schematic

10155-002

This applies voltage to the inputs of the unpowered ADA4096-2; however, no latch-up or damage occurs for input voltages up to 32 V. If slower throughput rates are required, the AD7920 can also be powered down between samples. The AD7920 draws a maximum of 5 μ W when powered down and 15 mW when powered up. The ADA4096-2 requires only 120 μ A under operational conditions. When operating at 5 V, this is only 0.6 mW. The ADP3336 draws only 1 μ A in the shutdown mode.

CIRCUIT DESCRIPTION

The circuit is a classic high-side current sensing circuit topology with a single sense resistor. The other four resistors (dual 1 k Ω /20 k Ω divider) are in a thin film network (for ratio matching) and are used to set the difference amplifier gain. This amplifies the difference between the two voltages seen across the sense resistor and rejects the common-mode voltage.

$$V_{OUT} = (V_A - V_B) (20 \text{ k}\Omega / 1 \text{ k}\Omega)$$

Figure 2 shows a simplified schematic of the ADA4096-2. The input stage comprises two differential pairs (Q1 to Q4 and Q5 to Q8) operating in parallel. When the input common-mode voltage approaches $V_{CC} - 1.5$ V, Q1 to Q4 shut down as I_1 reaches its minimum voltage compliance. Conversely, when the input common-mode voltage approaches $V_{EE} + 1.5$ V, Q5 to Q8 shut down as I_2 reaches its minimum voltage compliance. This topology allows for maximum input dynamic range because the amplifier can function with its inputs at 200 mV outside the rail (at room temperature).

As with any rail-to-rail input amplifier, V_{OS} mismatch between the two input pairs determines the CMRR of the amplifier. If the input common-mode voltage range is within 1.5 V of each rail, transitions between the input pairs are avoided, thus improving the CMRR by approximately 10 dB.

The ADA4096-2 inputs are protected from input voltage excursions up to 32 V outside each rail. This feature is of particular importance in applications with power supply sequencing issues that can cause the signal source to be active before the supplies to the amplifier are applied.

Figure 3 shows the input current limiting capability of the ADA4096-2 provided by low $R_{DS\text{ON}}$ internal series FETs (green curves) compared to using a 5 k Ω external series resistor with an unprotected op amp (red curves).

Figure 3 was generated with the ADA4096-2 in a unity-gain buffer configuration with the supplies connected to GND (or ± 15 V) and the positive input swept until it exceeds the supplies by 32 V. In general, input current is limited to 1 mA during positive overvoltage conditions and 200 μ A during negative undervoltage conditions. For example, at an overvoltage of 20 V, the ADA4096-2 input current is limited to 1 mA, providing a current limit equivalent to a series 20 k Ω resistor.

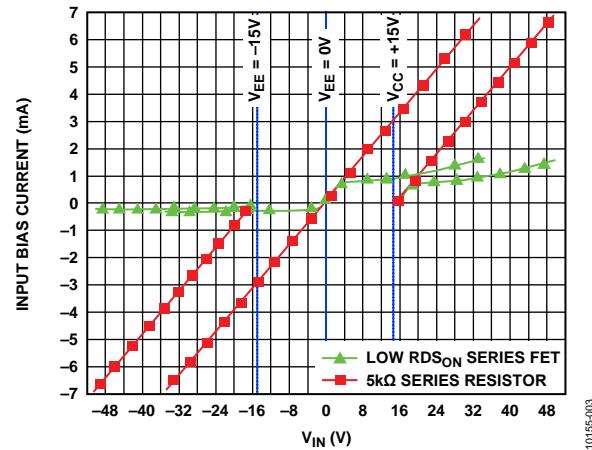


Figure 3. Input Current Limiting Capability

10155-003

Figure 3 also shows that the current limiting circuitry is active whether the amplifier is powered or not.

Figure 3 represents input protection under abnormal conditions only. The correct amplifier operation input voltage range (IVR) is specified in Table 2 to Table 4 of the ADA4096-2 data sheet.

The AD7920 is a 12-bit, high speed, low power, successive approximation ADC. The part operates from a single 2.35 V to 5.25 V power supply and features throughput rates up to 250 kSPS. The part contains a low noise, wide bandwidth track-and-hold amplifier that can handle input frequencies in excess of 13 MHz.

The conversion process and data acquisition are controlled using CS and the serial clock, SCLK, allowing the devices to interface with microprocessors or DSPs. The input signal is sampled on the falling edge of CS, and the conversion is initiated at this point. There are no pipeline delays associated with the part.

The [AD7920](#) uses advanced design techniques to achieve very low power dissipation at high throughput rates.

To enter power-down mode, the conversion process must be interrupted by bringing CS high anywhere after the second falling edge of SCLK, and before the tenth falling edge of SCLK. Once CS is brought high in this window of SCLKs, the part enters power-down mode, the conversion that was initiated by the falling edge of CS is terminated, and SDATA goes back into three-state. If CS is brought high before the second SCLK falling edge, the part remains in normal mode and does not power down. This avoids accidental power down due to glitches on the CS line.

To exit this mode of operation and power up the [AD7920](#) again, a dummy conversion is performed. On the falling edge of CS, the device begins to power up and continues to power up as long as CS is held low until after the falling edge of the tenth SCLK. The device is fully powered up once 16 SCLKs have elapsed, and valid data results from the next conversion.

If CS is brought high before the tenth SCLK falling edge, the [AD7920](#) goes back into power-down mode again. This avoids accidental power up due to glitches on the CS line or an inadvertent burst of eight SCLK cycles while CS is low. Although the device can begin to power up on the falling edge of CS, it powers down again on the rising edge of CS as long as it occurs before the tenth SCLK falling edge.

Further details regarding the timing can be found in the [AD7920](#) data sheet.

Test Results

An important measure of the performance of the circuit is the amount of noise in the final output voltage measurement.

Figure 4 shows a histogram of 10,000 measurement samples. This data was taken with the [CN-0241 Evaluation Board](#) connected to the [EVAL-SDP-CB1Z](#) SDP-B evaluation board. Details of the setup are described in the Circuit Evaluation and Test section.

The power supply was set to 3.0 V, and 10,000 samples of data were acquired at the maximum rate of 250 kSPS without having turned the output of the LDO off. Figure 4 shows the results of this acquisition. The peak-to-peak noise is approximately 2 LSBs, corresponding to about 0.3 LSB rms.

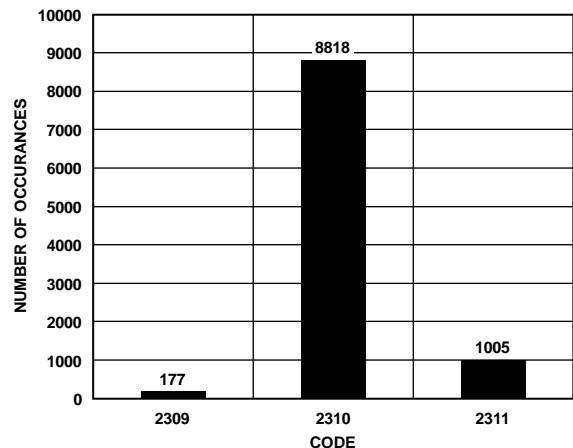


Figure 4. Histogram of Codes for 10,000 Samples Before Power Down

The SD shutdown pin connected to the [ADP3336](#) was then asserted low in the software causing the output of the LDO to turn off. After approximately 1 minute, the shutdown pin on the [ADP3336](#) was then asserted high, turning the output back on, and the same number of data samples were acquired. Figure 5 shows the results of this acquisition.

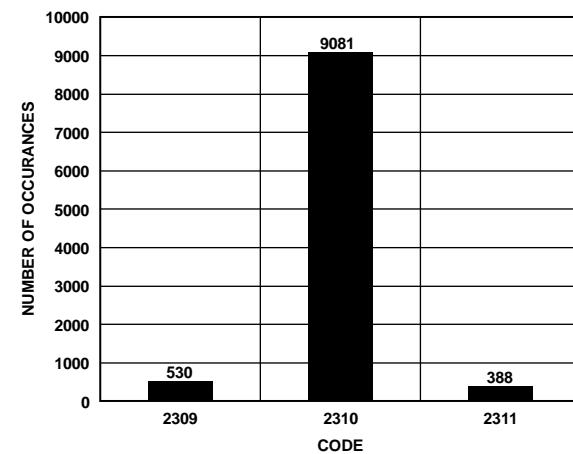


Figure 5. Histogram of Codes for 10,000 Samples After Power Down

Figure 5 shows that the output of the [ADA4096-2](#) did not latch during power down when the input was held high.

A complete design support package for this circuit note can be found at www.analog.com/CN0241-DesignSupport.

COMMON VARIATIONS

The circuit is proven to work with good stability and accuracy. This board is also compatible with the SDP-S controller board ([EVAL-SDP-CS1Z](#)).

A slight modification to the circuit shown in Figure 1 allows monitoring the current for input supply voltages up to 30 V. Rather than connect the +V pin of the [ADA4096-2](#) to 5 V from the [ADP3336](#), connect it directly to the input supply being monitored. In this configuration, the [ADA4096-2](#) is powered directly from the input supply.

CIRCUIT EVALUATION AND TEST

This circuit uses the [EVAL-CN0241-SDPZ](#) circuit board and the [EVAL-SDP-CB1Z](#) SDP-B controller board. The two boards have 120-pin mating connectors, allowing for the quick setup and evaluation of the performance of the circuit. The [EVAL-CN0241-SDPZ](#) board contains the circuit to be evaluated, as described in this note, and the SDP-B controller board is used with the CN0241 evaluation software to capture the data from the [EVAL-CN0241-SDPZ](#) circuit board.

Equipment Needed

The following equipment is needed:

- A PC with a USB port and Windows® XP, Windows Vista®, or Windows® 7 (32-bit)
- [EVAL-CN0241-SDPZ](#) circuit evaluation board
- [EVAL-SDP-CB1Z](#) SDP-B controller board
- CN0241 SDP evaluation software
- DC power supply capable of driving 6 V/1 A
- DC power supply capable of driving 5 V/2.5 A
- 2 Ω/12 W load resistor

Getting Started

Load the evaluation software by placing the CN0241 evaluation software CD in the CD drive of the PC. Using **My Computer**, locate the drive that contains the evaluation software.

Functional Block Diagram

See Figure 1 of this circuit note for the circuit block diagram and the [EVAL-CN0241-SDPZ-SCH-RevA.pdf](#) file for the circuit schematics. This file is contained in the [CN0241 Design Support Package](#).

Setup

Connect the 120-pin connector on the [EVAL-CN0241-SDPZ](#) circuit board to the CON A connector on the [EVAL-SDP-CB1Z](#) controller (SDP-B) board. Use Nylon hardware to firmly secure the two boards, using the holes provided at the ends of the 120-pin connectors. With power to the supply off, connect a 6 V power supply to the +6 V and GND pins on the board. If available, a 6 V wall wart can be connected to the barrel connector on the board and used in place of the 6 V power supply. Connect the USB cable supplied with the SDP-B board to the USB port on the PC. Do not connect the USB cable to the mini-USB connector on the SDP-B board at this time.

Connect the 5 V/2.5 A dc supply to +VIN and GND on J1 of the [EVAL-CN0241-SDPZ](#) board. Connect the 2 Ω/12 W load resistor to LOAD and GND of the [EVAL-CN0241-SDPZ](#) board.

Test

Apply power to the 6 V supply (or wall wart) connected to the [EVAL-CN0241-SDPZ](#) circuit board. Launch the evaluation software and connect the USB cable from the PC to the USB miniconnector on the SDP-B board.

Once USB communications are established, the SDP-B board can be used to send, receive, and capture serial data from the [EVAL-CN0241-SDPZ](#) board.

Turn the 5 V/2.5 A dc supply on when data is ready to be acquired. Adjust the voltage output accordingly to output the amount of current needed to be measured.

Figure 6 shows a screenshot of the CN0241 SDP evaluation software interface, and Figure 7 shows a screenshot of the [EVAL-CN0241-SDPZ](#) evaluation board. Information regarding the SDP-B board can be found in the [SDP-B User Guide](#).

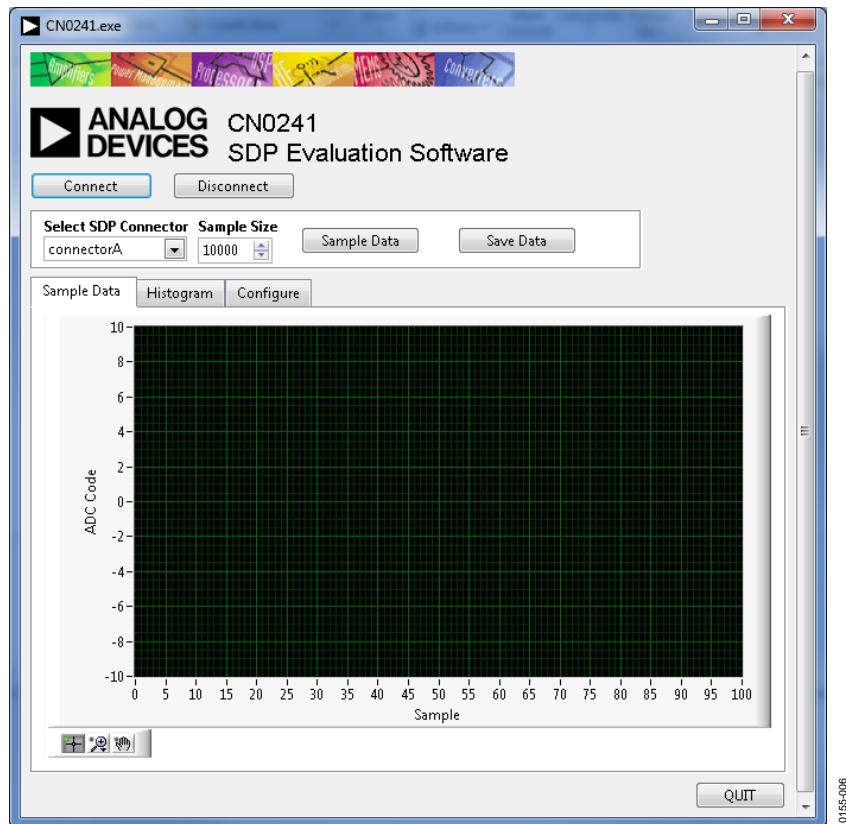


Figure 6. CN-0241 SDP Evaluation Software Interface

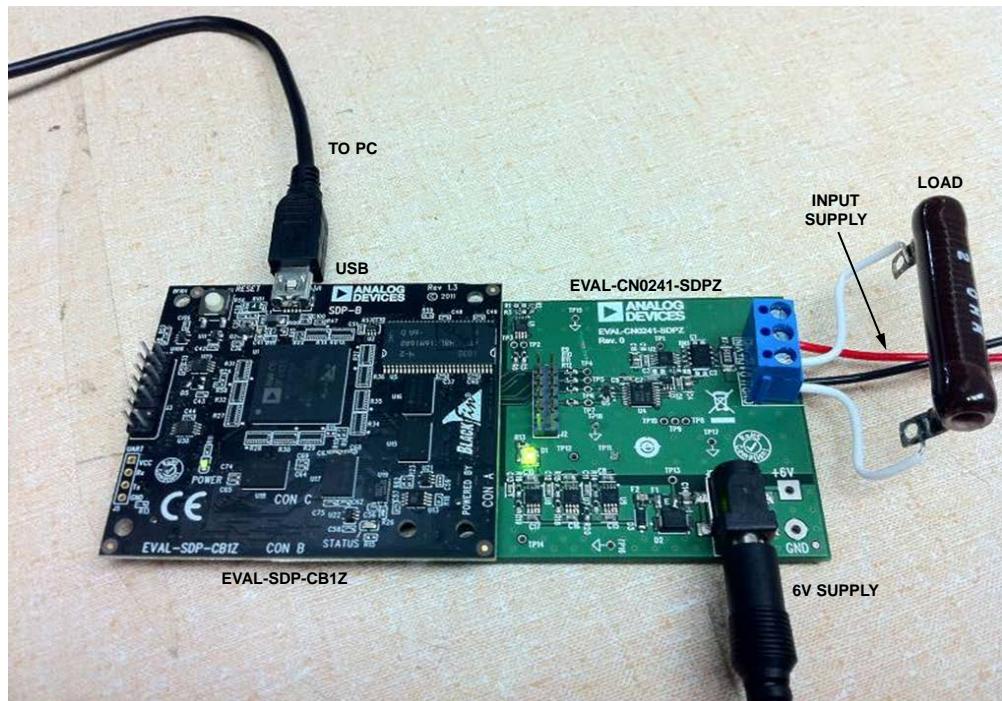


Figure 7. EVAL-CN0241-SDPZ Evaluation Board Connected to the SDP Board

LEARN MORE

CN0241 Design Support Package:

<http://www.analog.com/CN0241-DesignSupport>

SDP-B User Guide

Ardizzoni, John. *A Practical Guide to High-Speed Printed-Circuit-Board Layout*, Analog Dialogue 39-09, September 2005.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND"*, Analog Devices.

MT-035, *Op Amp Inputs, Outputs, Single-Supply, and Rail-to-Rail Issues*, Analog Devices.

MT-036 Tutorial, *Op Amp Output Phase-Reversal and Input Over-Voltage Protection*, Analog Devices.

MT-068 Tutorial, *Difference and Current Sense Amplifiers*, Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*, Analog Devices.

Data Sheets and Evaluation Boards

CN-0241 Circuit Evaluation Board (EVAL-CN0241-SDPZ)

System Demonstration Platform (EVAL-SDP-CB1Z)

ADA4096-2 Data Sheet

AD7920 Data Sheet

ADP3336 Data Sheet

REVISION HISTORY**5/12—Rev. 0 to Rev. A**

Changes to Circuit Function and Benefits Section and Figure 1 1
Changes to Figure 6 5

1/12—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.

©2012 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.



Данный компонент на территории Российской Федерации**Вы можете приобрести в компании MosChip.**

Для оперативного оформления запроса Вам необходимо перейти по данной ссылке:

<http://moschip.ru/get-element>

Вы можете разместить у нас заказ для любого Вашего проекта, будь то серийное производство или разработка единичного прибора.

В нашем ассортименте представлены ведущие мировые производители активных и пассивных электронных компонентов.

Нашей специализацией является поставка электронной компонентной базы двойного назначения, продукции таких производителей как XILINX, Intel (ex.ALTERA), Vicor, Microchip, Texas Instruments, Analog Devices, Mini-Circuits, Amphenol, Glenair.

Сотрудничество с глобальными дистрибуторами электронных компонентов, предоставляет возможность заказывать и получать с международных складов практически любой перечень компонентов в оптимальные для Вас сроки.

На всех этапах разработки и производства наши партнеры могут получить квалифицированную поддержку опытных инженеров.

Система менеджмента качества компании отвечает требованиям в соответствии с ГОСТ Р ИСО 9001, ГОСТ Р В 0015-002 и ЭС РД 009

Офис по работе с юридическими лицами:

105318, г.Москва, ул.Щербаковская д.3, офис 1107, 1118, ДЦ «Щербаковский»

Телефон: +7 495 668-12-70 (многоканальный)

Факс: +7 495 668-12-70 (доб.304)

E-mail: info@moschip.ru

Skype отдела продаж:

moschip.ru
moschip.ru_4

moschip.ru_6
moschip.ru_9