

# AN-EVAL-1HS01G-1-200W

## 200 W 24 V 6 A & 12 V 5 A SMPS demonstrator with ICE1HS01G-1

Application Note

## About this document

### Scope and purpose

This document is a 200 W 24 V 6 A & 12 V 5 A 280 V<sub>AC</sub> input off-line half bridge LLC resonant converter demonstrator board using Infineon ICE1HS01G-1.

### Intended audience

This document is intended for users of the ICE1HS01G-1 who wish to design a system of high efficiency, simple in design, low cost and high reliable in half bridge (HB) LLC resonant converter for application of LED/OLED/LCD/PDP TV, AC-DC adapter and audio SMPS.

## Table of Contents

<b>About this document .....</b>	<b>1</b>
<b>Table of Contents.....</b>	<b>1</b>
<b>1      Abstract .....</b>	<b>3</b>
<b>2      Demonstrator board.....</b>	<b>3</b>
<b>3      Specifications of demonstrator board .....</b>	<b>5</b>
<b>4      Features of ICE1HS01G-1.....</b>	<b>5</b>
<b>5      Circuit description.....</b>	<b>6</b>
<b>6      Circuit Operation .....</b>	<b>7</b>
6.1      Startup Operation .....	7
6.2      Output Voltage Regulation.....	8
<b>7      Protection Features.....</b>	<b>9</b>
7.1      V <sub>CC</sub> Under Voltage Protection .....	9
<b>8      Circuit Diagram and Components List .....</b>	<b>12</b>
8.1      Schematics.....	12

---

**Abstract**

8.2	PCB Layout.....	13
8.3	Components List .....	14
<b>9</b>	<b>Transformer Construction.....</b>	<b>17</b>
9.1	Mains Transformer .....	17
<b>10</b>	<b>Electrical Test Results .....</b>	<b>19</b>
10.1	Efficiency Measurements.....	19
10.2	Zero Voltage Switching.....	19
10.3	Soft Start .....	20
10.4	Over Current Protection .....	21
10.5	Over Load Protection.....	21
10.6	Output Short Circuit Protection .....	22
10.7	Mains Under Voltage Protection.....	23
10.8	Burst Mode Operation at No Load.....	23
10.9	Dynamic Load Response .....	24
<b>11</b>	<b>References .....</b>	<b>25</b>
<b>Revision History.....</b>		<b>25</b>

## Abstract


## 1 Abstract

The demo board described in this paper is a 200W half bridge LLC resonant converter using LLC controller ICE1HS01G-1, which is an 8-pin LLC controller developed by Infineon Technologies. ICE1HS01G-1 is specially designed for applications of switch mode power supplies used in LED / OLED / LCD / PDP TV, AC/DC adapter and Audio system.

ICE1HS01G-1 is an 8-pin DSO-8 controller IC, the PCB layout can be easily implemented. Moreover, it includes all necessary control strategies for HB LLC resonant converter. ICE1HS01G-1 allows the designer to choose suitable operation frequency range by programming the oscillator with an external resistor. And the built-in soft-start function to limit both the inrush current and the overshoot of output voltage is also provided. In addition, ICE1HS01G-1 performs all necessary protection functions in HB LLC resonant converters. All of these make ICE1HS01G-1 an outstanding product for HB LLC resonant converter in the market.

## 2 Demonstrator board

The 200W half bridge LLC resonant converter demo board with ICE1HS01G-1 is implemented as shown in Figure 1. The LLC stage's full load efficiency reaches >93.9%.

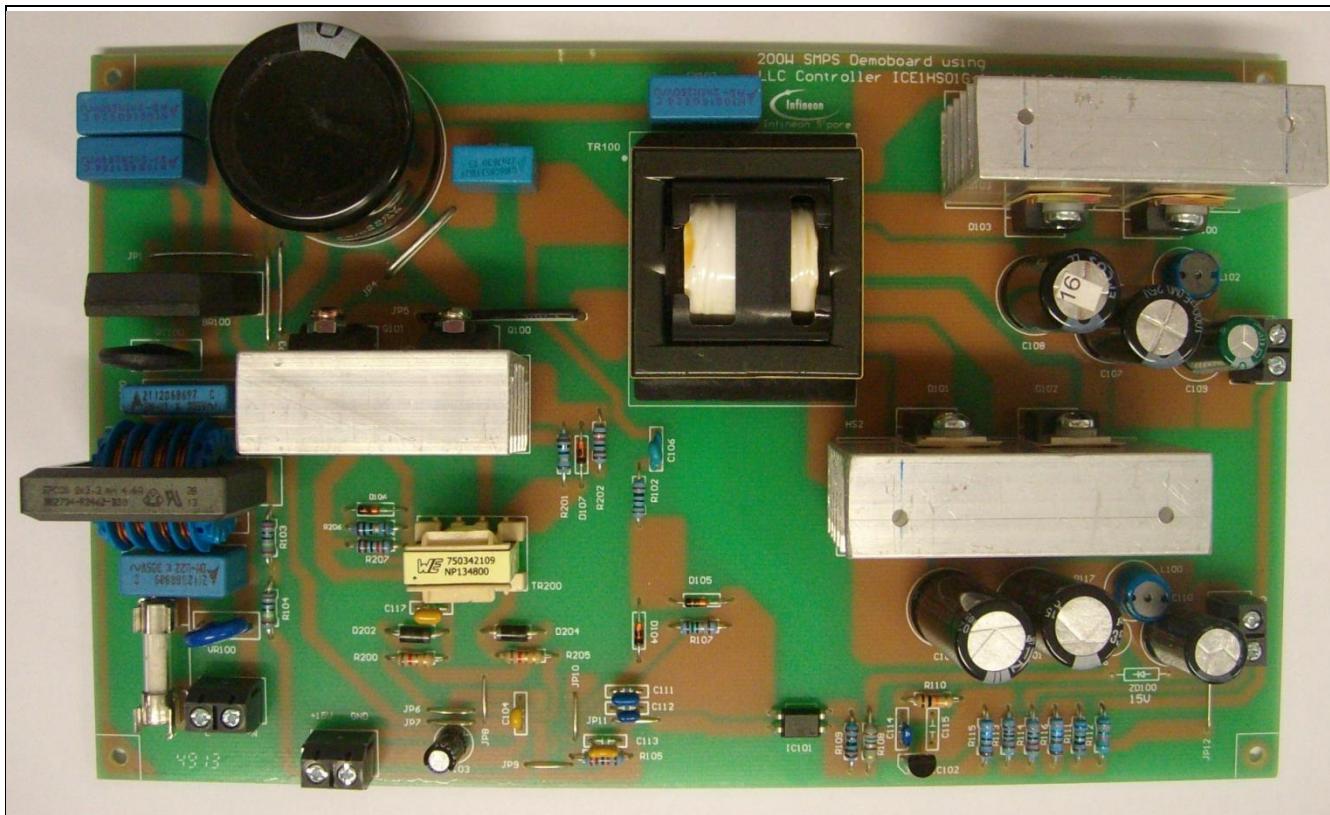

**Figure 1 EVAL-1HS01G-1-200W half bridge LLC resonant converter (top view)**

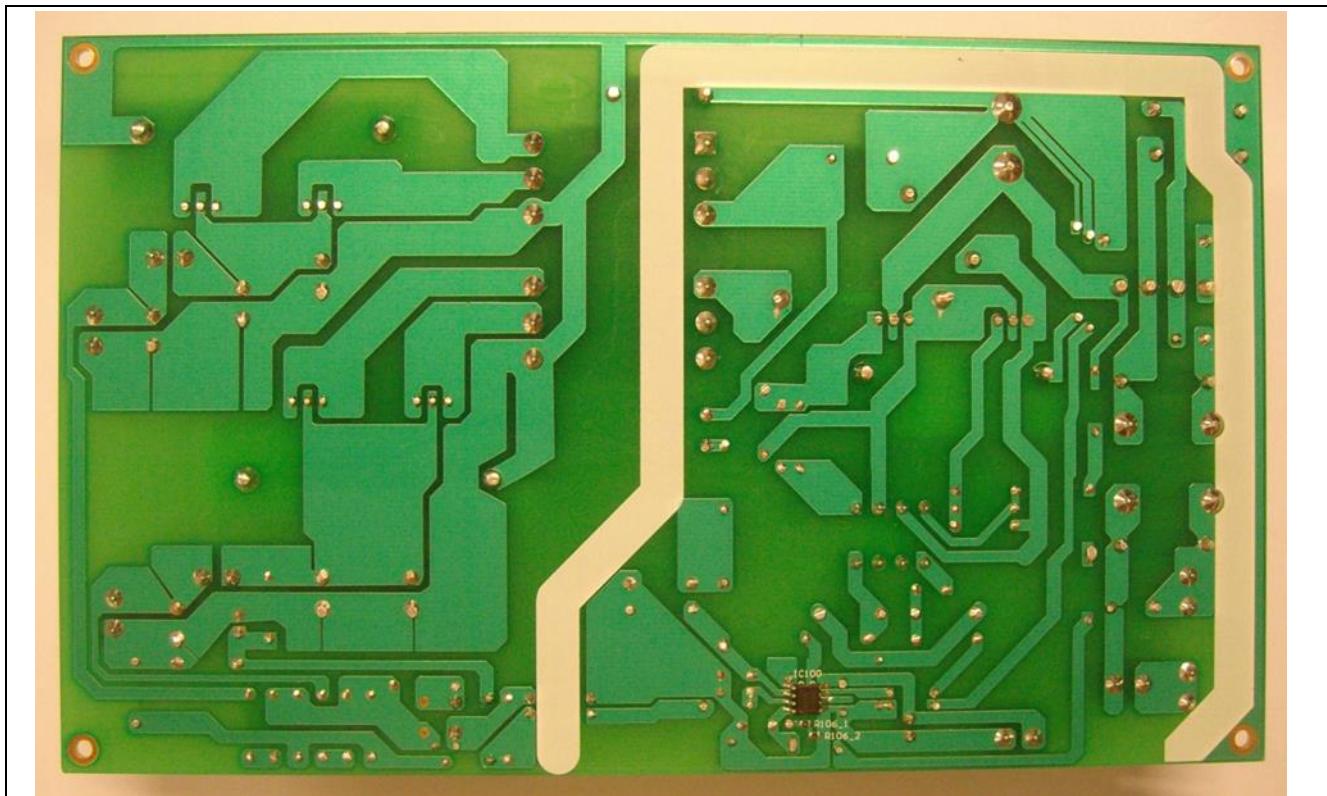


Figure 2 EVAL-1HS01G-1-200W half bridge LLC resonant converter (bottom view)

## Specifications of demonstrator board

### 3 Specifications of demonstrator board

**Table 1 Specifications of EVAL-1HS01G-1-200W**

Nominal AC Input voltage	280 V <sub>AC</sub>
Nominal DC Input voltage	380 V <sub>DC</sub>
Mains under voltage protection point	285 V <sub>DC</sub>
Auxiliary power supply for IC V <sub>CC</sub>	15 V <sub>DC</sub>
Nominal output full load	24 V 6 A, 12 V 5 A
Switching frequency	95kHz @ 24 V 6 A, 12 V 5 A and 380 V <sub>DC</sub> input
Form factor case size (L x W x H)	200mm x 120mm x 32mm

### 4 Features of ICE1HS01G-1

**Table 2 Features of ICE1HS01G-1**

Maximum 600kHz switching frequency
Adjustable minimum switching frequency with high accuracy
50% duty cycle
Mains input under voltage protection with adjustable hysteresis
Two levels of over-current protection: frequency shift and latch off
Open-loop/over load protection with extended blanking time
Built-in digital and nonlinear soft start
Adjustable restart time during fault protection period

---

## Circuit description

### 5 Circuit description

In actual application, the LLC stage is used to follow a PFC pre-regulator. In this demo board, in order to simplify and speed up the LLC controller's feature evaluation, the conventional bridge rectifier BR100, instead of PFC, is used to provide high input DC voltage for the downstream LLC stage. Thus, around 280 V<sub>AC</sub> input voltage is recommended to feed this demo board, and accordingly 380 V<sub>DC</sub> voltage across bulk capacitor C100 can be achieved.

The AC line input side comprises the input fuse FUSE100 as over-current protection. The X2 Capacitors CX100, CX101 and Choke L101 and Y1 capacitors CY100 and CY101 forms a main filter to minimize the feedback of RFI into the main supply. NTC resistor RT100 is placed in series with input to limit the initial peak inrush current. After the bridge rectifier BR100, together with a smoothing capacitor C100, a voltage of 300 V<sub>DC</sub> to 400 V<sub>DC</sub> is provided, depending on mains input voltage, to simulate the real operation condition with front end PFC pre-regulator.

Also, the bulk capacitor C100 can be directly connected to an external DC power supply, thus the 380 V<sub>DC</sub> can be obtained. This measure makes sense when the customers want to evaluate the LLC stage's efficiency.

The second stage is a half bridge LLC resonant converter, operating in zero voltage switching mode. The controller ICE1HS01G-1 is an 8 pin LLC controller, which incorporates the necessary functions to drive the half bridge's high side and low side MOSFETs (Q100 and Q101) by a 50% duty cycle with dead time. The switching frequency can be changed by ICE1HS01G-1 to regulate the output voltage against the load and input voltage variations. During operation, the primary MOSFETs Q100 and Q101 are turned-on under ZVS condition and the secondary rectifier diodes D100~D103 are turned-on and turned-off under ZCS condition. Hence high power conversion efficiency can be achieved.

The Driver Circuit can be implemented by cost-effective pulse transformer. As shown in Figure-7, Pulse transformer TR200 is used to transmit the driver signal to MOSFETs for isolation purpose.

The mains transformer TR100 uses the magnetic integration approach, incorporating the resonant series and shunt inductances. Thus, no additional external coils are needed for the resonance. The transformer configuration chosen for the secondary winding is center-tapped, and the output rectifiers D100~D103 are schottky diodes, in order to limit the power dissipation.

In case of a short circuit, the current flowing through the primary winding is detected by the lossless circuit (C106, C111, D104, D105, R102, and R107) and the resulting signal is fed into CS Pin.

In case of overload, the voltage on CS pin will overpass an internal threshold 0.8V that triggers a protection mode which keeping the current flowing in the circuit at a safe level. In addition, the blanking time and the restart time can be adjusted by external components.

## Circuit Operation

# 6 Circuit Operation

## 6.1 Startup Operation

The controller ICE1HS01G-1 is targeting at applications with auxiliary power supply. In most cases, a front-end PFC pre-regulator with a PFC controller is used in the same system.

After IC supply voltage is higher than 12V, and if the voltage on VINS pin is higher than 1.25V, IC will start switching with soft start. The soft start function is built inside the IC with a digital manner. During soft start, the switching frequency of the MOSFET is controlled internally by changing the current  $I_{SS}$  instead of by the feedback voltage. The charging current  $I_{SS}$  during soft start, which determines the switching frequency, is reduced step by step as shown in product datasheet [1]. The maximum duration of soft start is 32ms with 1ms for each step. Figure 3 illustrates the actual switching frequency vs start time when  $R_{FMIN}=25k\Omega$ . During soft start, the frequency starts from 209 kHz, and step by step drops to normal operation point.

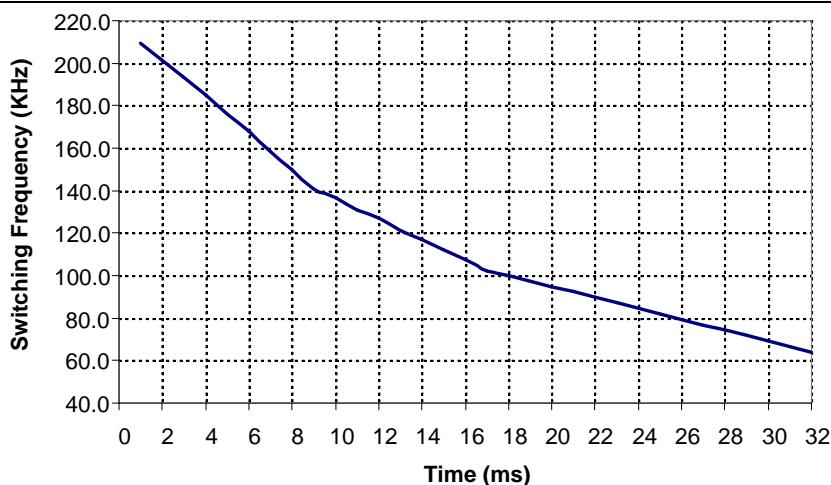


Figure 3 Switching frequency during soft start @  $R_{Fmin}=25k\Omega$

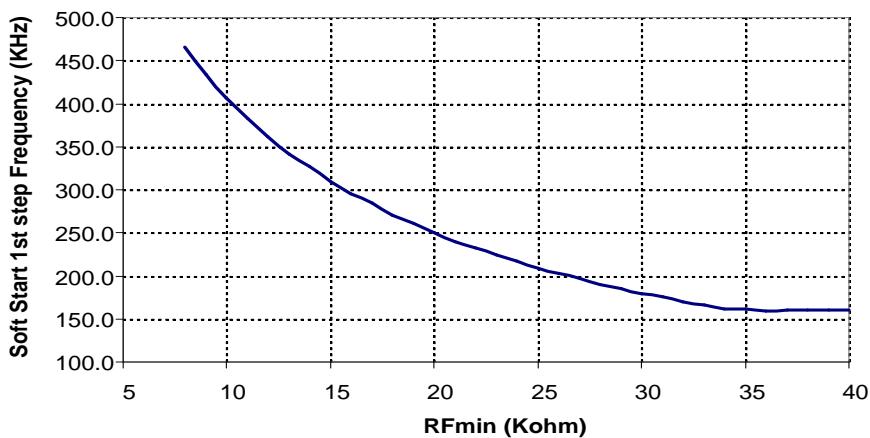


Figure 4 Soft start 1<sup>st</sup> step switching frequency vs  $R_{Fmin}$

The soft start 1<sup>st</sup> step switching frequency, maximum frequency during soft start, is also closely related to the minimum switching frequency fixed by external RFmin resistance. Figure 4 illustrates the relationship between the 1<sup>st</sup> step frequency and  $R_{Fmin}$ .


During soft start, the overload protection is disabled because FB voltage is high.

## Circuit Operation

### 6.2 Output Voltage Regulation

The minimum switching frequency is a very important factor to guarantee the LLC topology output voltage regulation at low line input and full load condition. ICE1HS01G-1 allows the minimum switching frequency easily programmed by connecting an external resistor  $R_{FMIN}$  between FMIN pin and ground.


The FMIN pin provides a precise 1.5V reference. The resistor  $R_{FMIN}$ , connected from FMIN pin to GND, determines the current ( $I_{FMIN}$ ) flowing out of FMIN pin. Around one-tenth of  $I_{FMIN}$  is defined as the minimum charging current ( $I_{chg\_min}$ ), which in turn defines the minimum switching frequency. The maximum switching frequency during normal operation and the switching frequency variation range during soft start and over current protection are all related to this current flowing out of FMIN pin, which is discussed in the product datasheet [1].

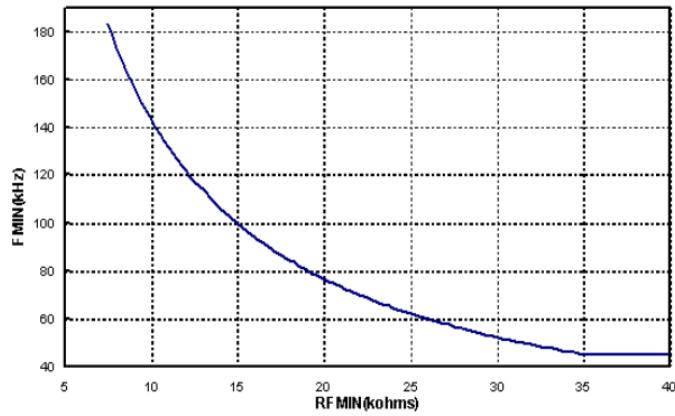

**Figure 5 Minimum switching frequency VS  $R_{FMIN}$**

The output load information is fed into the controller through feedback voltage  $V_{FB}$ . Inside the IC, the feedback (FB) pin is connected to the 5V voltage source through a pull-up resistor  $R_{FB}$ . Outside the IC, this pin is connected to the collector of opto-coupler. Normally, a ceramic capacitor  $C_{FB}$  can be put between this pin and ground for signal smoothing purpose, also  $C_{FB}$  is used to determine the extended blanking time for over load protection, which will be discussed in section 7.3.

If the output load is increased, and consequently  $V_{FB}$  is higher, ICE1HS01G-1 will reduce the switching frequency to regulate the output voltage and vice versa. The regulation of switching frequency is achieved by changing the charging current  $I_{FB}$ . The relationship between  $I_{FB}$  and  $V_{FB}$  can be found in product datasheet [1]. The effective range of feedback voltage  $V_{FB}$  is from 1V to 4V. Figure 6 graphs the relationship between the actual switching frequency and feedback voltage  $V_{FB}$  when  $R_{FMIN}=25k\Omega$ .

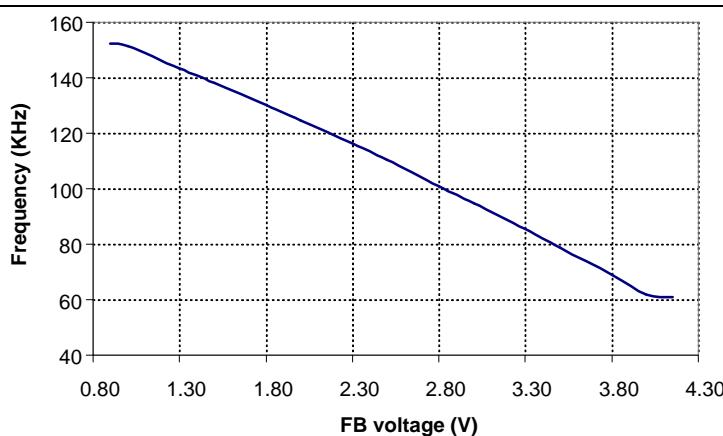

**Figure 6 Switching frequency VS feedback @  $R_{Fmin}=25k\Omega$**

## Protection Features

# 7 Protection Features

## 7.1 V<sub>CC</sub> Under Voltage Protection

The controller ICE1HS01G-1 is targeting at applications with auxiliary power supply. In most cases, a front-end PFC pre-regulator with a PFC controller is used in the same system.

The controller starts to operate when the supply voltage V<sub>CC</sub> reaches the on-threshold, typically 12V. The minimum operating voltage after turn-on, V<sub>VCCoff</sub>, is typically 11V. The maximum supply voltage V<sub>VCCmax</sub> is 18V. It is suggested that IC is supplied with a regulated dc power supply for stable operation. At the same time, a small bypass filter capacitor is suggested to be put between V<sub>CC</sub> and GND pins, as closely as possible.

## 7.2 Over Current Protection

Current sense pin in ICE1HS01G-1 is only for protection purpose. ICE1HS01G-1 features two-level over current protection. In case of over-load condition, the lower OCP level, 0.8V, will be triggered, the switching frequency will be increased according to the duration and power of the over load. The higher OCP level, 1.6V, is used to protect the converter if transformer winding is shorted. When V<sub>CS</sub> reaches 1.6V, the IC will be latched immediately.

If V<sub>CS</sub> is higher than 0.8V, IC will boost up the switching frequency. If V<sub>CS</sub> is lower than 0.75V, IC will resume to normal operation gradually. If V<sub>CS</sub> is always higher than 0.8V for 1.5ms, the frequency will rise to its maximum level and vice versa.

To sum up, ICE1HS01G-1 will increase the switching frequency to limit the resonant current in case of temporary over-load and will also decrease the switching frequency to its normal value after over-load condition goes away.

## 7.3 Over Load Protection

In case of output over load or open control loop fault, the FB voltage will increase to its maximum level. If FB voltage is higher than V<sub>FBH</sub> and this condition last longer than a fixed blanking time of T<sub>OLP</sub> (20ms), the IC will start the extended blanking timer. The extended blanking timer is realized by charging and discharging the filter capacitor C<sub>FB</sub> via the internal pull up resistor R<sub>FB</sub> and switch Q<sub>FB</sub>. Accordingly the voltage across C<sub>FB</sub> varies between V<sub>FBL</sub> and V<sub>FBH</sub>.

The time needed for C<sub>FB</sub> being charged from V<sub>FBL</sub> to V<sub>FBH</sub> can be calculated as:

$$t_{chg\_olp} = -\ln\left(\frac{V_{dd} - V_{FBH}}{V_{dd} - V_{FBL}}\right) \cdot R_{FB} \cdot C_{FB}$$

The time needed for C<sub>FB</sub> being discharged from V<sub>FBH</sub> to V<sub>FBL</sub> can be calculated as:

$$t_{dischg\_olp} = \ln\left(\frac{V_{FBH}}{V_{FBL}}\right) \cdot R_{QFB} \cdot C_{FB}$$

Thanks to an internal counter, the total extended blanking time can be calculated as:

$$t_{ext\_blank} = 512 \cdot (t_{chg\_olp} + t_{dischg\_olp})$$

where R<sub>QFB</sub> is switch Q<sub>FB</sub>'s on resistance, R<sub>QFB</sub>=900ohm, V<sub>FBH</sub>=4.5V, V<sub>FBL</sub>=0.5V.

## Protection Features

For example, if  $C_{FB}$  is 680pF,  $t_{chg\_olp}$  is about 30us,  $t_{dischg\_olp}$  is about 1.4us,  $t_{ext\_blank}$  is about 16ms.

If the converter returns to normal operation during the extended blanking time, IC will reset all faults timer to zero and return to normal operation.

After IC enters into OLP, both switches will be stopped. However, the IC remains active and will try to start with soft start after an adjustable period. This period is realized by charging and discharging the capacitor  $C_{INS}$ , connected to VINS pin, for  $N_{OLP\_R}$  times ( $N_{OLP\_R}=2048$ ), accordingly the voltage across  $C_{INS}$  varies between  $V_{INSH}$  and  $V_{INSL}$ .

The charging and discharging time of  $C_{INS}$  can be approximated as:

$$t_{charging} = -R_{eq} \cdot C_{INS} \cdot \ln \left( \frac{V_{BUS} \cdot \frac{R_{eq}}{R_{INS1}} + I_{INST} \cdot R_{eq} - V_{INSH}}{V_{BUS} \cdot \frac{R_{eq}}{R_{INS1}} + I_{INST} \cdot R_{eq} - V_{INSL}} \right)$$

$$t_{discharging} = -R_{eq2} \cdot C_{INS} \cdot \ln \left( \frac{V_{BUS} \cdot \frac{R_{eq2}}{R_{INS1}} - V_{INSL}}{V_{BUS} \cdot \frac{R_{eq2}}{R_{INS1}} - V_{INSH}} \right)$$

where  $R_{eq}$  is the equivalent resistance for paralleling of  $R_{INS1}$  and  $R_{INS2}$ ,

$$R_{eq} = R_{INS1} // R_{INS2}$$

$R_{eq2}$  is the equivalent resistance for paralleling of  $R_{INS1}$ ,  $R_{INS2}$  and  $R_{Q3}$  (900ohm typically).

$$R_{eq2} = R_{INS1} // R_{INS2} // R_{Q3}$$

$I_{INST}$  is an internal constant current source  $I_{INST}=680\mu A$ .

$V_{INSL}$  and  $V_{INSH}$  is the min. and max voltage at VINS pin:  $V_{INSL}=0.5V$ ,  $V_{INSH}=4.5V$ .

For example, if assume  $R_{INS1}=5M\Omega$ ,  $R_{INS2}=22k\Omega$ , then  $t_{charging}=158\mu s$ ,  $t_{discharging}=44\mu s$ .

IC will repeat the charging and discharging process for  $N_{OLP\_R}$  times ( $N_{OLP\_R}=2048$ ). After that, IC will turn off the switches for both charging and discharging. In addition, the current source for hysteresis will be turned on and another blanking time of  $T_{BL\_VINS}$  ( $T_{BL\_VINS}=20ms$ ) will be added so that VINS pin fully recovers and represents the bus voltage information. IC will start the soft start after the additional blanking time in case  $V_{VINS}$  is higher than the  $V_{VINSon}$ .

The total restart time can be calculated as:

$$t_{restart} = 2048 \cdot (t_{charging} + t_{discharging}) + 20ms$$

## 7.4 Mains Under Voltage Protection

The working range of mains input voltage needs to be specified for LLC resonant converter. It is important for the controller to have input voltage sensing function and protection feature, which allow the IC to stop switching when the input voltage drops below the specified range and restart with soft start when the input voltage resumes to its normal level. The mains input voltage sensing circuit is shown in product datasheet [1]. Thanks to the internal current source  $I_{hys}$  (12 $\mu A$ ) connected between VINS pin and Ground, an adjustable hysteresis between the on and off threshold of mains input voltage can be created as:

## Protection Features

$$V_{hys} = R_{INS1} \cdot I_{hys}$$

The mains input voltage is divided by  $R_{INS1}$  and  $R_{INS2}$ . If the on and off threshold for mains input voltage is  $V_{mainon}$  and  $V_{mainoff}$ , the resistors  $R_{INS1}$  and  $R_{INS2}$  can be selected as:

$$R_{INS1} = \frac{V_{mainon} - V_{mainoff}}{I_{hys}}, \quad R_{INS2} = R_{INS1} \cdot \frac{V_{VINSon}}{V_{mainoff} - V_{VINSon}}$$

where  $I_{hys}=12\mu A$ ,  $V_{VINSon}=1.25V$ .

For example, if  $R_{INS1}=5M\Omega$  and  $R_{INS2}=22k\Omega$ , the calculated  $V_{mainon}=345V$ ,  $V_{mainoff}=285V$ .

## 7.5 Open Load Protection

At very light load condition, eg. open load, the designed maximum frequency may not be high enough to regulate the output voltage, the output voltage may loss control and cause damages. In order to avoid this issue, the feedback signal  $V_{FB}$  is continuously monitored. When  $V_{FB}$  drops below  $V_{FB\_off}$  (typical 0.2V), the switching signal is disabled after a fixed blanking time,  $T_{FB}$  (typical 200ns).  $V_{FB}$  will then rise as  $V_{OUT}$  starts to decrease due to no switching signal. Once  $V_{FB}$  exceeds the threshold  $V_{FB\_on}$  (typical 0.3V), IC resumes to normal operation.

## Circuit Diagram and Components List

## 8 Circuit Diagram and Components List

## 8.1 Schematics


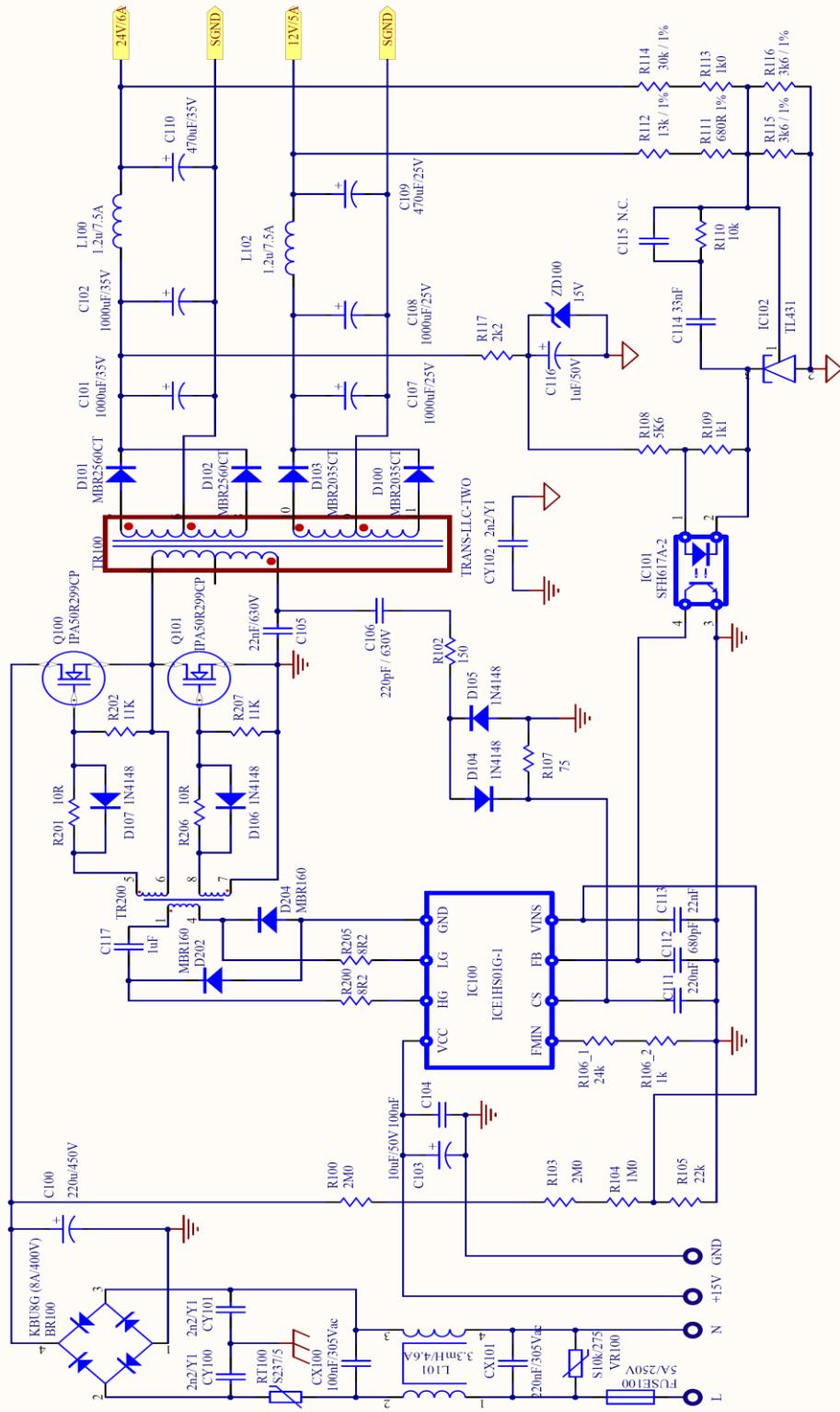



Figure 7 Schematics of 200W half bridge LLC resonant

## Circuit Diagram and Components List

## 8.2 PCB Layout

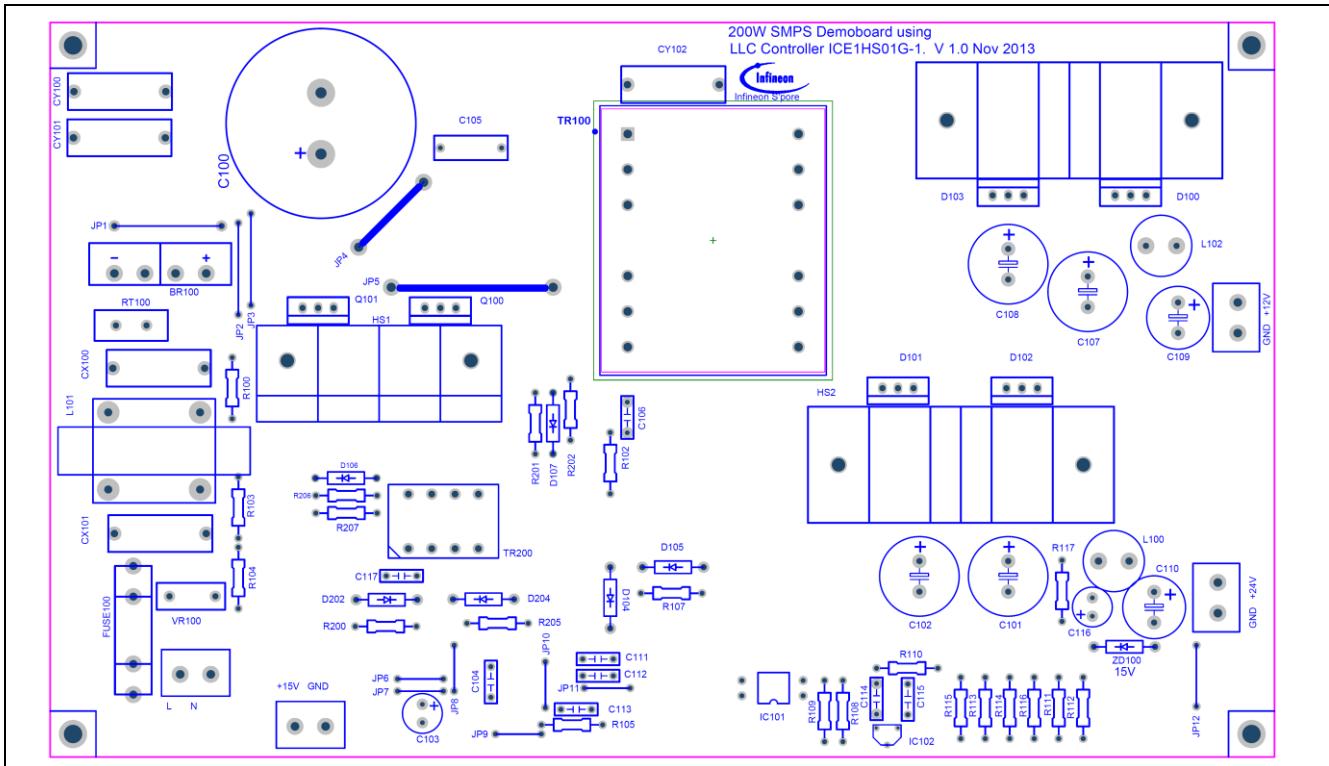

**Figure 8 Component side - View from component side**

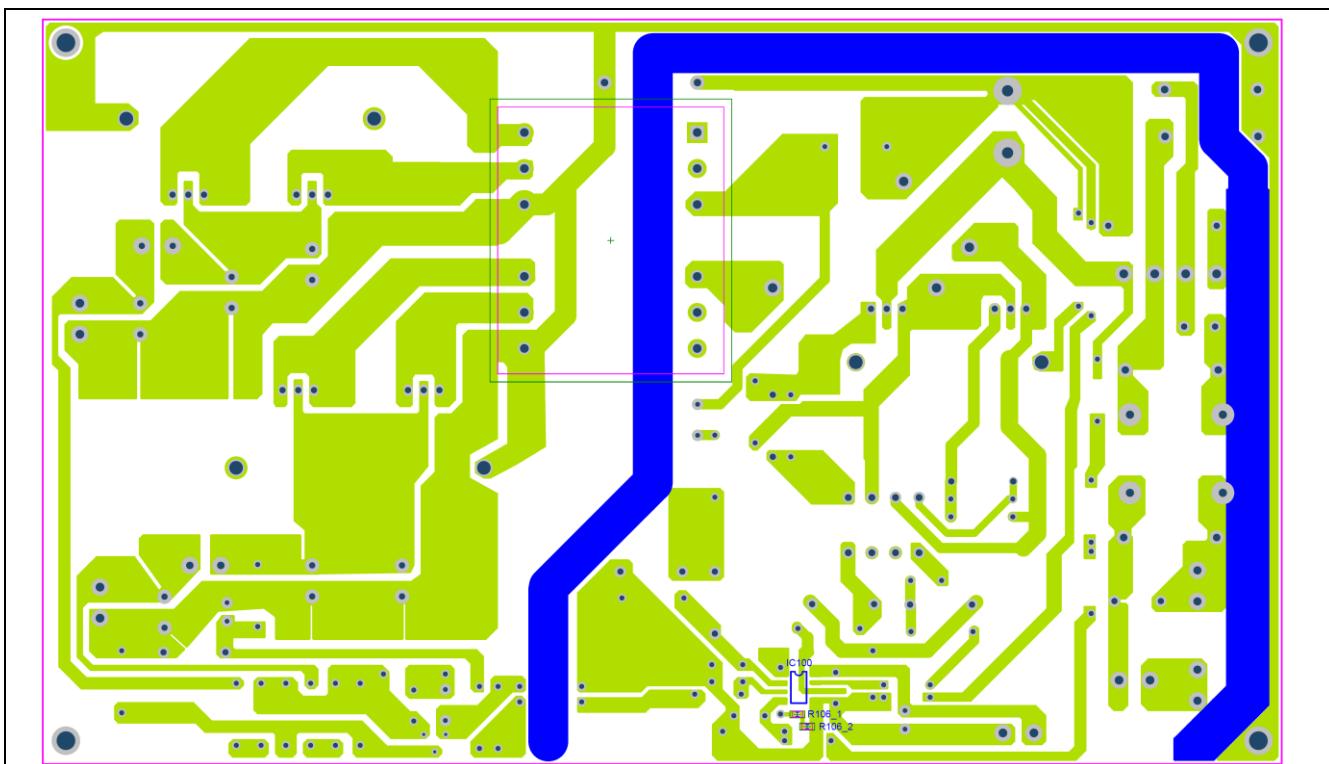

**Figure 9 Solder side - View from solder side**

## Circuit Diagram and Components List

### 8.3 Components List

Table 3 Bill of Materials

Item	Circuit code	Part value	Description	Supplier / Part No.
1	BR100	KBU8G (8A / 400V)	BRIDGE RECTIFIER	
2	C100	220µF/450V	Aluminum Electrolyte	EPCOS / B43304C5227M000
3	C101	1000µF/35V	Aluminum Electrolyte	
4	C102	1000µF/35V	Aluminum Electrolyte	
5	C103	10µµF/50V	Aluminum Electrolyte	EPCOS / B41821A6106M000
6	C104	100nF/50V	CERAMIC	
7	C105	22nF/630V	CERAMIC	EPCOS / B32621A6223J000
8	C106	220pF / 630V	CERAMIC	
9	C107	1000µF/25V	Aluminum Electrolyte	
10	C108	1000µF/25V	Aluminum Electrolyte	
11	C109	470µF/25V	Aluminum Electrolyte	
12	C110	470µF/35V	Aluminum Electrolyte	
13	C111	220nF/50V	CERAMIC	
14	C112	680pF/50V	CERAMIC	
15	C113	22nF/50V	CERAMIC	
16	C114	33nF/50V	CERAMIC	
17	C115	N.C.	CERAMIC	
18	C116	1µF/50V	Aluminum Electrolyte	
19	C117	1µF/50V	CERAMIC	
20	CX100	100nF/305 V <sub>AC</sub>	CERAMIC	
21	CX101	220nF/305 V <sub>AC</sub>	CERAMIC	EPCOS / B32922C3224K000
22	CY100	2n2/500Vac Y1	CERAMIC	EPCOS / B81123C1222M000
23	CY101	2n2/500Vac Y1	CERAMIC	EPCOS / B81123C1222M000
24	CY102	2n2/500Vac Y1	CERAMIC	EPCOS / B81123C1222M000
25	D100	MBR2035CT	SCHOTTKY DIODE	Vishay / MBR2035CT
26	D101	MBR2560CT	SCHOTTKY DIODE	Vishay / MBR2560CT
27	D102	MBR2560CT	SCHOTTKY DIODE	Vishay / MBR2560CT
28	D103	MBR2035CT	SCHOTTKY DIODE	Vishay / MBR2035CT
29	D104	1N4148	DIODE	
30	D105	1N4148	DIODE	
31	D106	1N4148	DIODE	
32	D107	1N4148	DIODE	
33	D202	MBR160	SCHOTTKY DIODE	
34	D204	MBR160	SCHOTTKY DIODE	
35	FUSE100	5A/250V	RESISTOR FUSE	
36	IC100	ICE1HS01G-1	Resonant-Mode	INFINEON / ICE1HS01G-1

**Circuit Diagram and Components List**

			Controller	
37	IC101	SFH617A-2	OPTO COUPLER	
38	IC102	TL431	ERROR AMPLIFIER	
39	L100	1.2µH/7.5A	CHOKE	
40	L101	3.3mH/4.6A	COMMON MODE CHOKE	EPCOS / B82734R2462B30
41	L102	1.2µH/7.5A	CHOKE	
42	Q100	IPA50R299CP	POWER MOSFET	INFINEON / IPA50R299CP
43	Q101	IPA50R299CP	POWER MOSFET	INFINEON / IPA50R299CP
44	R100	2M / 1%	RESISTOR	
45	R102	150R	RESISTOR	
46	R103	2M / 1%	RESISTOR	
47	R104	1M / 1%	RESISTOR	
48	R105	22k / 1%	RESISTOR	
49	R106_1	24k / 1%, 0805	RESISTOR	
50	R106_2	1k / 1%	RESISTOR	
51	R107	75R	RESISTOR	
52	R108	5k6	RESISTOR	
53	R109	1k1	RESISTOR	
54	R110	10k / 1%	RESISTOR	
55	R111	680R / 1%	RESISTOR	
56	R112	13k / 1%	RESISTOR	
57	R113	1k0 / 1%	RESISTOR	
58	R114	30k / 1%	RESISTOR	
59	R115	3k6 / 1%	RESISTOR	
60	R116	3k6 / 1%	RESISTOR	
61	R117	2k2	RESISTOR	
62	R200	8R2	RESISTOR	
63	R201	10R	RESISTOR	
64	R202	11K	RESISTOR	
65	R205	8R2	RESISTOR	
66	R206	10R	RESISTOR	
67	R207	11K	RESISTOR	
68	RT100	S237/5	Thermister	EPCOS / B57237S509M000
69	TR100	TRANS-LLC-TWO	LLC Transformer	Wurth Electronics Midcom Inc. (Model:750342784)
70	TR200	Pulse Transformer	Pulse transformer	Wurth Electronics Midcom Inc. (Model:750342109)
71	VR100	S10k/275	VDR	EPCOS / B72210S271K101
72	ZD100	15V	Zener diode	
73	JP1,JP2,JP3, JP4,JP5,JP6,	Jumper	Jumper	

**Circuit Diagram and Components List**

	JP7, JP8, JP9, JP10, JP11, JP12			
74	HS1	For Q100, Q101	Heatsink	
75	HS2	For D101, D102	Heatsink	
76	HS3	For D100, D103	Heatsink	
77	CN1	For AC	2-pin connector	
78	CN2	For 15V	2-pin connector	
79	CN3	For 12V	2-pin connector	
80	CN4	For 24V	2-pin connector	

## Transformer Construction

# 9 Transformer Construction

## 9.1 Mains Transformer

- Bobbin: type ER34
- Core: TP4 ER34 from TDG
- Primary inductance:  $636\mu\text{H}\pm5\%$ , Gapped between Pin3 and Pin5 (measured at 50kHz)
- Leakage inductance:  $100\mu\text{H}\pm5\%$ , measured between Pin3 and Pin5 by shorting (Pin 8 & 10 and Pin 12 & 14) or (Pin 8& 9 and Pin 12 & 13) (measured at 100kHz)
- Manufacturer and part number : Wurth Electronics Midcom 750342784

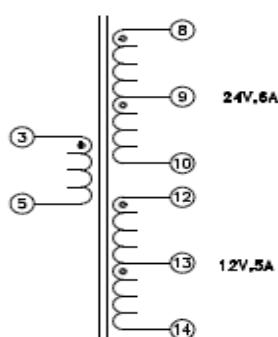


Figure 10 LLC resonant transformer electrical diagram

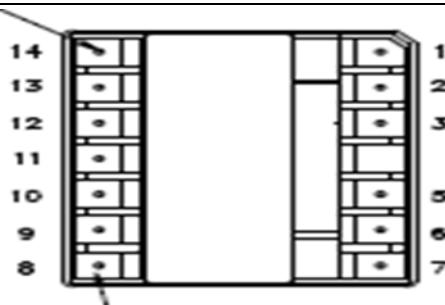


Figure 11 LLC resonant transformer complete - bottom view

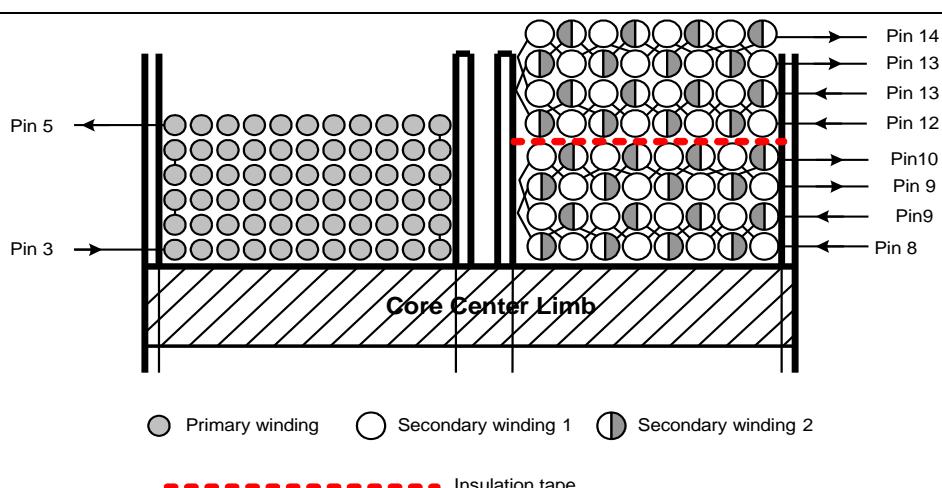


Figure 12 LLC resonant transformer winding position

## Transformer Construction

Table 4 LLC resonant transformer winding characteristics

Pins	winding	turns	wire
3~5	primary	34	7*0.20
8~9	Secondary 1	4	19*0.20
9~10	Secondary 2	4	19*0.20
12~13	Secondary 3	2	19*0.20
13~14	Secondary 4	2	19*0.20

## 9.2 Pulse Transformer

- Bobbin: E16/8/5, Vertical version from TDG
- Core: E16/8/5 TP4 from TDG
- Manufacturer and part number : Wurth Electronics Midcom 750342109

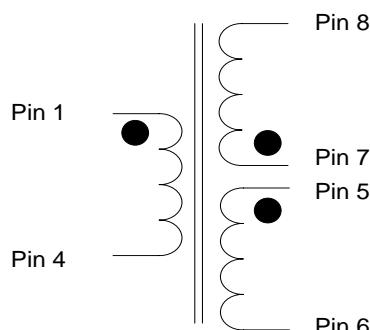


Figure 13 Pulse Transformer electrical diagram

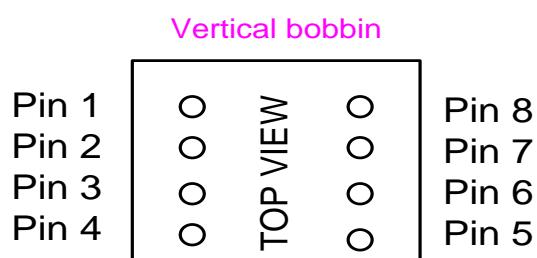


Figure 14 Pulse transformer complete - top view

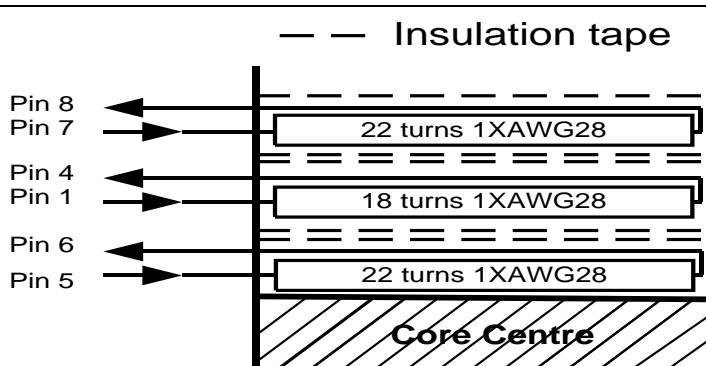


Figure 15 Pulse transformer winding position

## Electrical Test Results

# 10 Electrical Test Results


## 10.1 Efficiency Measurements

Table 5 shows the output voltage measurements at the nominal input voltage 380 V<sub>DC</sub>, with different load conditions. The input voltage 380 V<sub>DC</sub> is supplied from a high voltage DC power supply.

**Table 5 Efficiency measurements @ input voltage =380 V<sub>DC</sub>**

Load(%)	V <sub>out1</sub> (V)	I <sub>out1</sub> (A)	V <sub>out2</sub> (V)	I <sub>out2</sub> (A)	P <sub>out</sub> (W)	V <sub>in</sub> (V)	I <sub>in</sub> (A)	P <sub>in</sub> (W)	V <sub>cc</sub> (V)	I <sub>cc</sub> (A)	P <sub>cc</sub> (W)	Eff. (%)
100%	24.02	6.01	11.80	5.00	203.31	379.9	0.57	216.20	14.18	0.0199	0.28	93.91%
82%	23.99	5.00	11.82	4.00	167.30	379.9	0.47	177.53	14.18	0.0200	0.28	94.09%
65%	23.96	4.00	11.83	3.01	131.45	379.9	0.37	139.39	14.18	0.0202	0.29	94.11%
50%	23.97	3.01	11.82	2.50	101.77	379.9	0.28	108.04	14.18	0.0203	0.29	93.94%
47%	23.93	3.01	11.84	2.00	95.83	379.9	0.27	101.78	14.18	0.0203	0.29	93.90%
29%	23.89	2.01	11.86	1.00	59.89	379.9	0.17	64.13	14.18	0.0205	0.29	92.98%
20%	23.93	1.20	11.84	1.00	40.57	379.9	0.12	44.14	14.18	0.0206	0.29	91.30%
15%	23.89	1.01	11.86	0.51	30.08	379.9	0.09	33.17	14.18	0.0207	0.29	89.90%
10%	23.92	0.60	11.84	0.51	20.35	379.9	0.06	23.36	14.18	0.0207	0.29	86.00%
5%	23.90	0.30	11.85	0.25	10.15	379.9	0.03	12.88	14.18	0.0208	0.30	77.02%

The power losses due to IC and driver circuit are both included. In addition, the efficiency values were measured after 30 minutes of warm-up at full load.

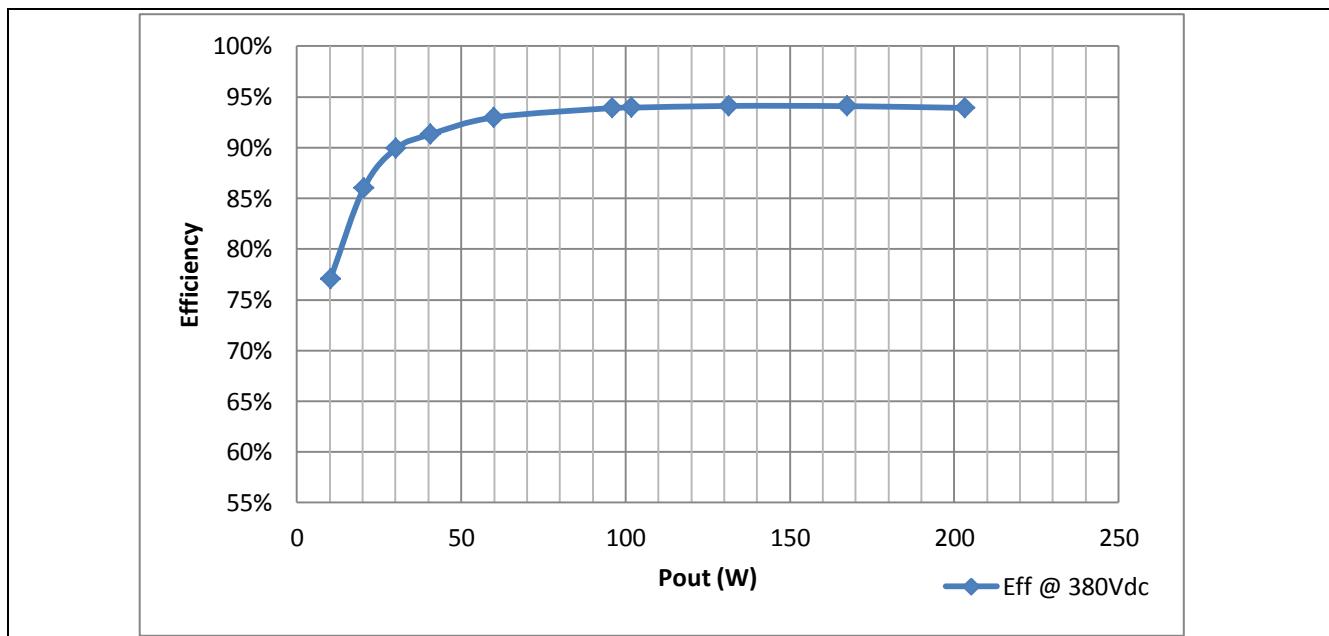

**Figure 16 LLC stage efficiency**

## 10.2 Zero Voltage Switching

## Electrical Test Results

The LLC system can achieve ZVS over a very wide range of load.

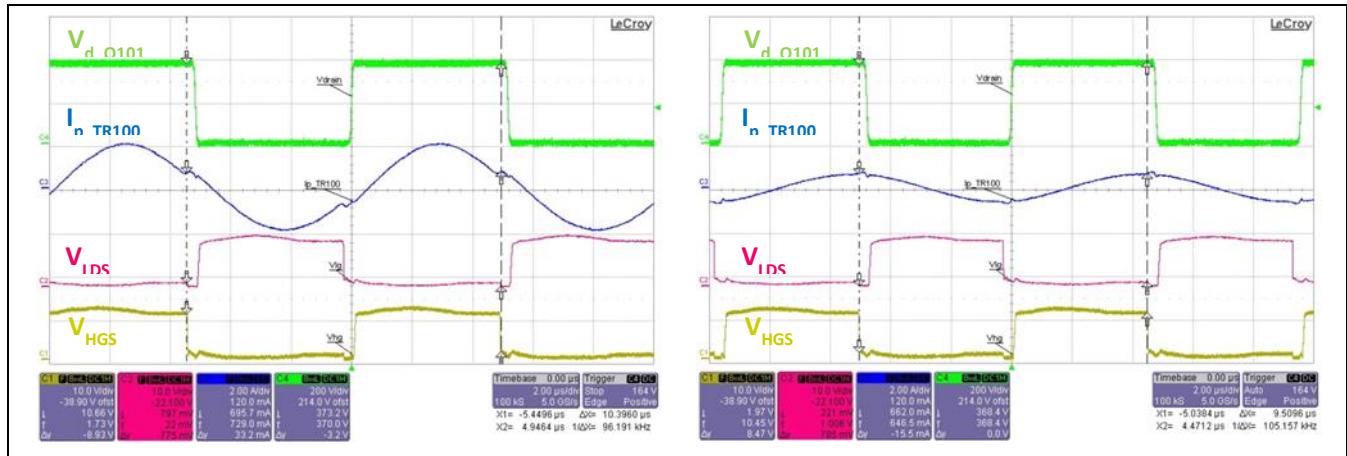


Figure 17 Zero Voltage switching (Left: @ 380 V<sub>DC</sub> input voltage and 100% full load, Right : @ 380 V<sub>DC</sub> input voltage and 10% full load)

## 10.3 Soft Start

During start-up at full load or no load, the primary resonant current is strictly limited, and the 24 V output voltage smoothly rises to its regulated value. The overshoot is less than 10%, the start-up time is less than 30ms.


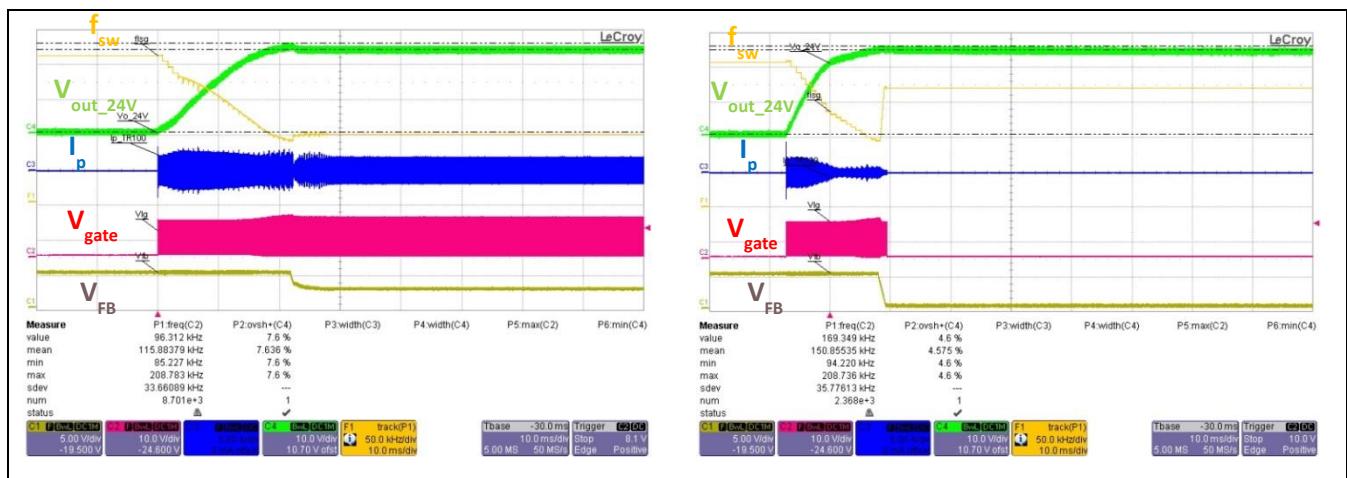


Figure 18 Soft start at full load and no load (Left: Soft start @ 380 V<sub>DC</sub> input voltage and full load, Right : Soft start @ 380 V<sub>DC</sub> input voltage and no load)

## Electrical Test Results

### 10.4 Over Current Protection


Figure 19 shows the over current protection. Two kinds of OCP are available. The 1<sup>st</sup> is  $V_{CS} > 0.8$  V and the switching frequency increase according to the exceeded duration. Then it would return to normal switching frequency when  $V_{CS} < 0.75$  V (left side waveform). The 2<sup>nd</sup> one is  $V_{CS} > 1.6$  V, the system enters latch mode (right side waveform).

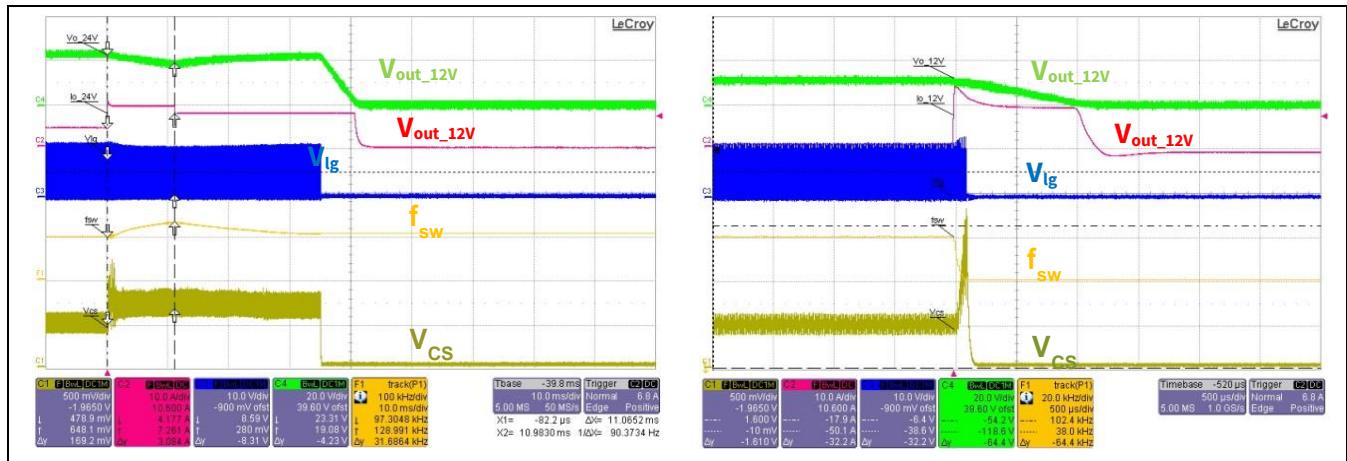

**Figure 19 Over Current Protection (Left : 12 V @ 5 A, 24 V @ 6 A - 9 A - switching frequency increase when  $V_{CS} > 0.8$  V and then drop to normal when  $V_{CS} < 0.75$  V. The system enters AR after over load protection reached. Right : 24 V @ 6 A, 12 V short circuit - system enter OCP latch mode when the  $V_{CS} > 1.6$  V.)**

### 10.5 Over Load Protection


Blanking time in case of over load protection can be adjusted as discussed before, the charging time  $t_{chg\_olp}$  and discharging time  $t_{dischq\_olp}$  of  $C_{FB}$  is 31.6 $\mu$ s and 1.62 $\mu$ s respectively, this measured result is closely equal to the calculated result which is mentioned at section 7.3.

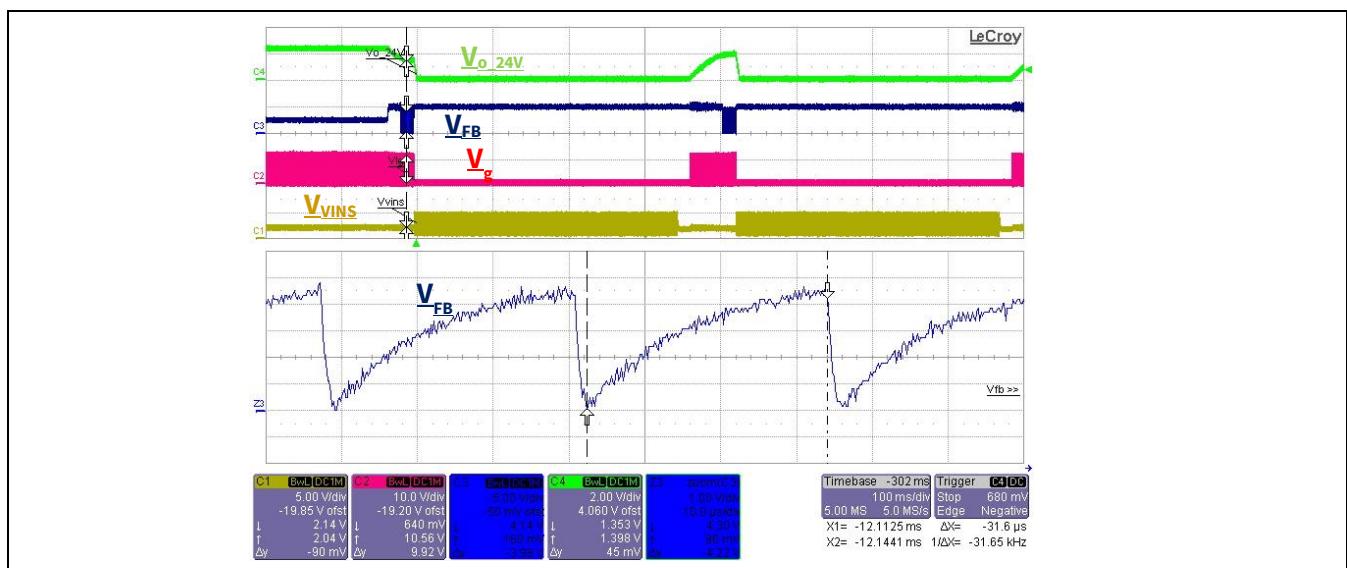

**Figure 20 Adjustable extended blanking time in case of over load protection**

Restart time in case of over load protection can also be adjusted as discussed before, the charging time  $t_{charge}$  and discharging time  $t_{discharge}$  of  $C_{vins}$  is 118.4 $\mu$ s and 51.8 $\mu$ s respectively, this measured result is closely equal to the calculated result which is mentioned at section 7.3.


## Electrical Test Results

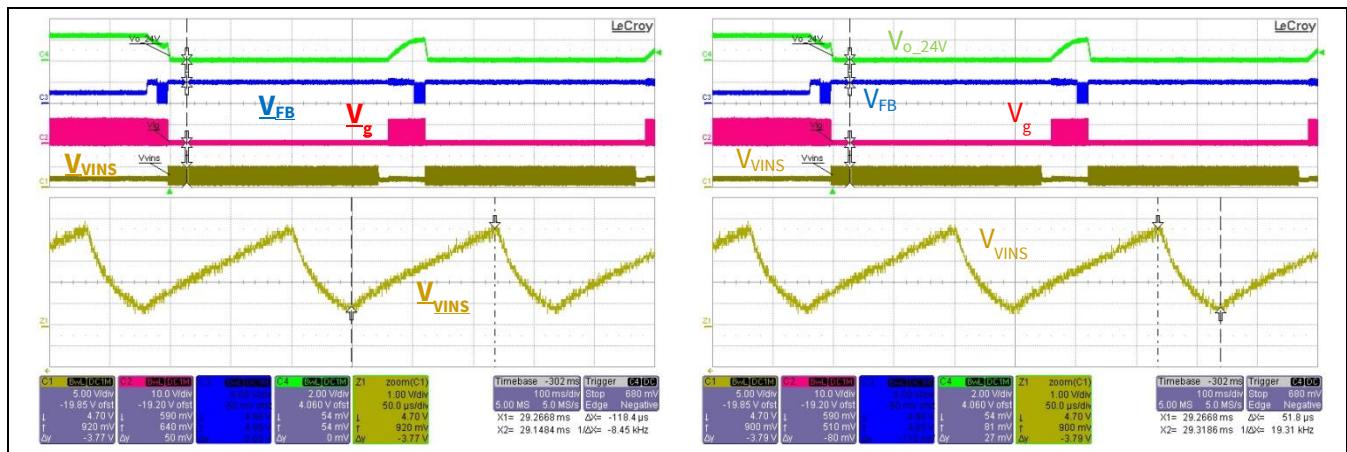

**Figure 21 Adjustable restart time in case of over load protection (Left :  $C_{VINS}$  charging time, Right :  $C_{VINS}$  discharging time)**

## 10.6 Output Short Circuit Protection

When the output load is short circuit,  $V_{FB}$  jumps to a higher value. When this condition lasts longer than the internal fixed blanking time 20ms, the extended adjustable blanking time will be initiated. After these two blanking times the IC will enter restart mode and stops switching if the short circuit condition still exists. After an adjustable restart time plus an internal fixed restart time 20ms, the IC resumes to normal operation with soft start. During soft start, the over load protection is disabled. When soft start process completed, if the output short circuit condition still exists, IC will enter auto restart mode again. When the output short circuit condition disappears, IC will resume to normal operation and the 24 V output voltage is established again.

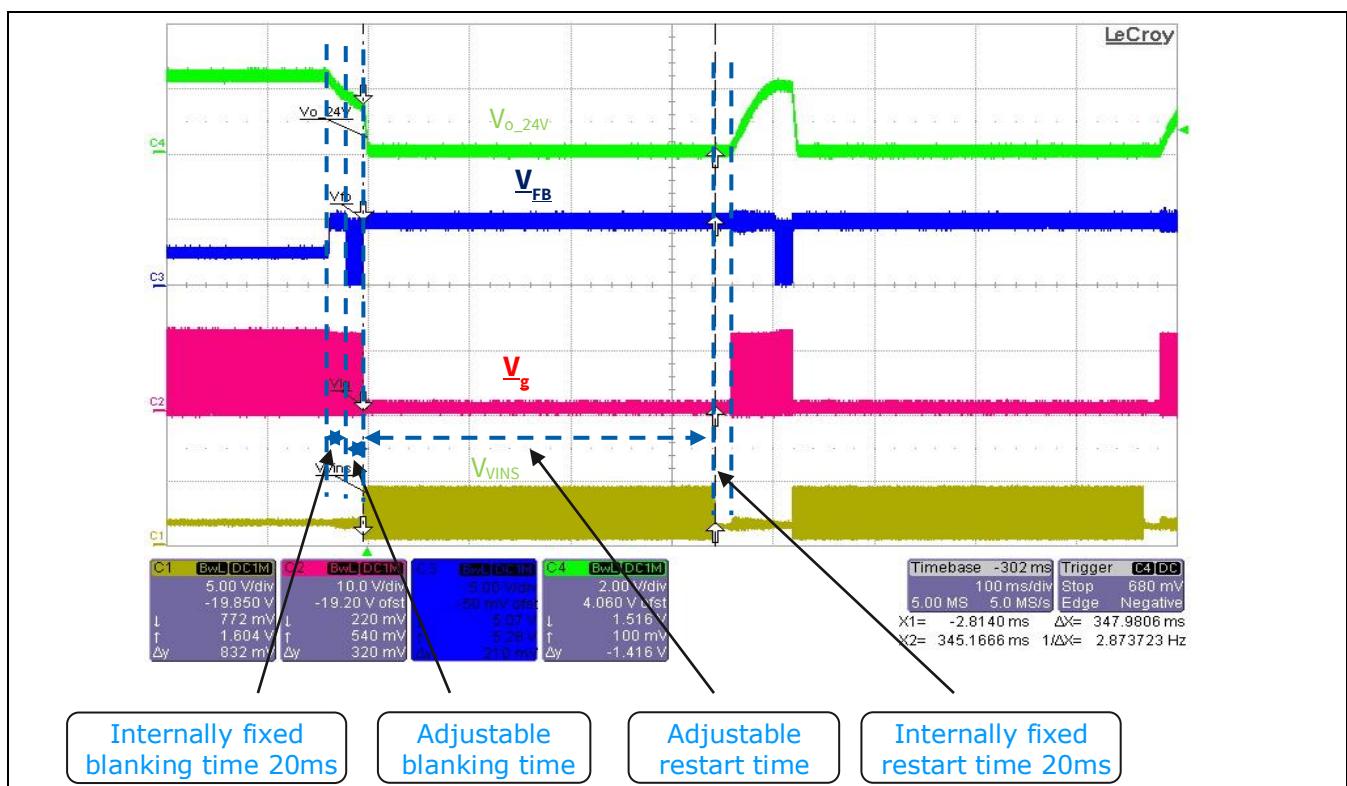


**Figure 22 Output short circuit protection**

## Electrical Test Results

## 10.7 Mains Under Voltage Protection


When  $V_{bus}$  drops lower than 285 V<sub>DC</sub>, IC stops switching; When  $V_{bus}$  rises up to 356 V<sub>DC</sub>, IC starts normal operation after a 500.8us blanking time. These measured results are closely equal to the calculated results mentioned at section 7.4.

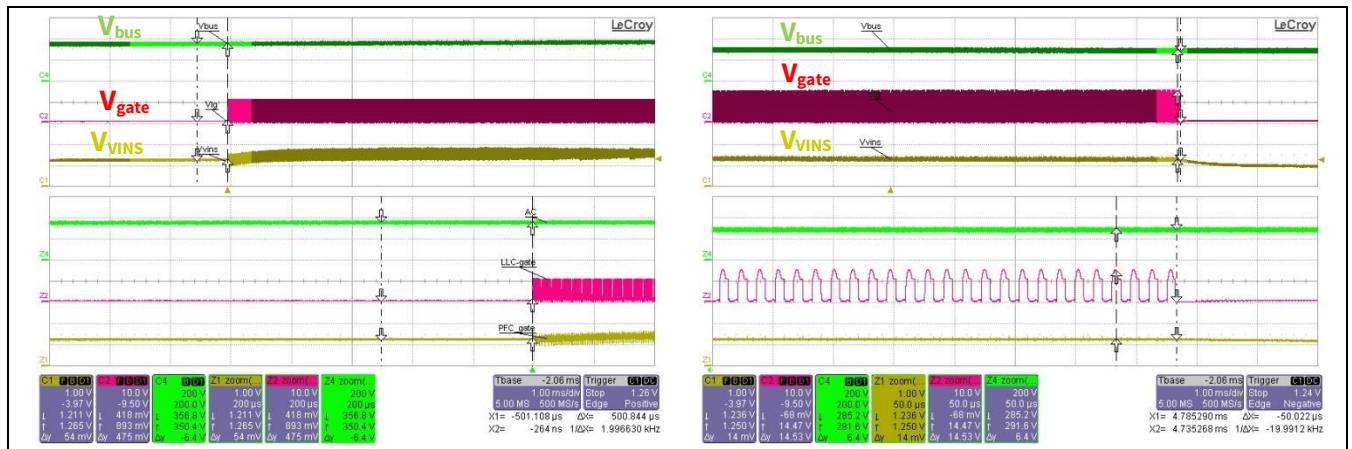

**Figure 23 Mains under voltage protection (Left : IC starts operation when Vbus resumes to normal value, Right : IC stops switching when Vbus drops to designed value)**

## 10.8 Burst Mode Operation at No Load

Burst mode operation is implemented in ICE1HS01G-1 to avoid possible over output voltage issue in case of light load or no load operation. When  $V_{FB}$  drops below  $V_{FB\_off}$  (measured value 0.180 V), the switching signal will be disabled.  $V_{FB}$  will then rise as  $V_{out}$  starts to decrease due to no switching signal. Once  $V_{FB}$  exceeds the threshold  $V_{FB\_on}$  (measured value 0.285 V), IC resumes to normal operation.

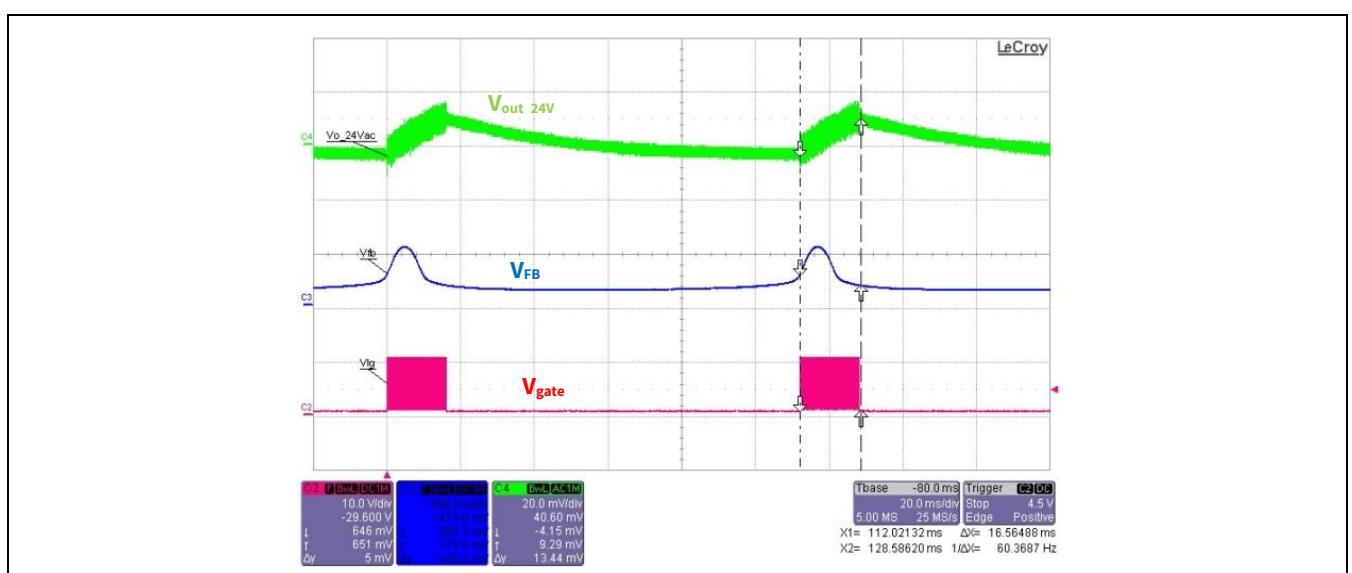

**Figure 24** Burst mode operation

## 10.9 Dynamic Load Response

Figure 25 shows the dynamic behavior of this demo board during a load variation from around 10% to 100% full load on one output, with the other output at its full load. The output voltage ripple of 24 V and 12 V are both less than 5%.

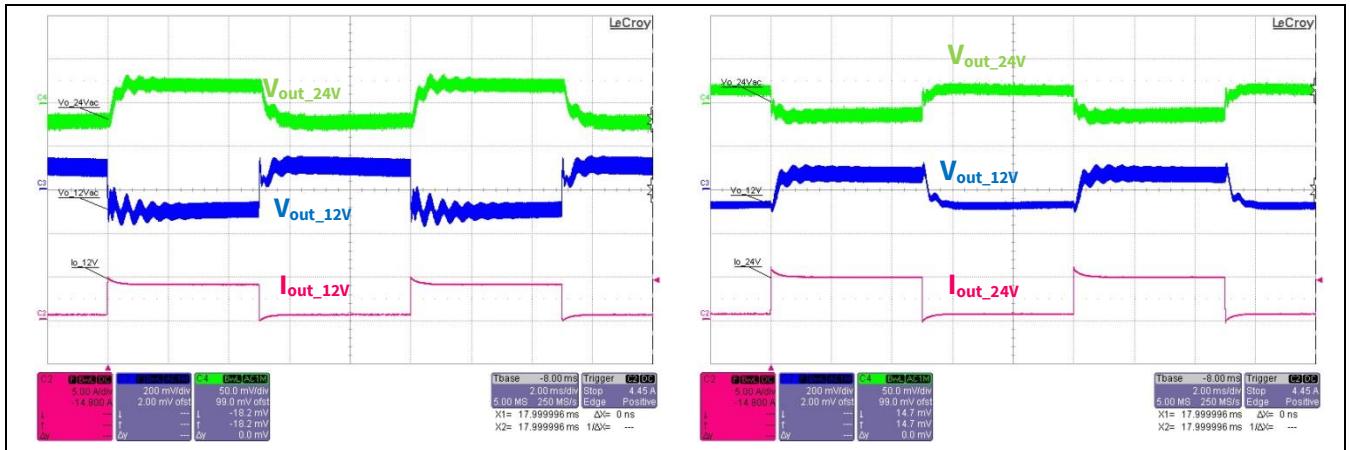


Figure 25 Dynamic load response (Left : 24 V @ 6 A, 12 V @ 0.5 A - 5 A, Right : 24 V @ 0.5 A - 6 A, 12 V @ 5 A)

---

## References

### 11 References

- [1] [Datasheet ICE1HS01G-1](#) Half-Bridge Resonant Controller, Infineon Technologies AG, 2011
- [2] [Application Note ANPS0031 -ICE1HS01G](#) Half Bridge LLC Resonant Converter Design using ICE1HS01G, Infineon Technologies, 2009
- [3] RW ERICKSON, D MAKSIMOVIC: 'Fundamentals of power electronics' (Kluwer Academic Publishers, 2001), pp. 705–755
- [4] B Yang: 'Topology investigation for front end DC/DC power conversion for distributed power system', PhD thesis, Virginia Polytechnic Institute and State University, 2003
- [5] Mingping Mao, Dimitar Tchobanov, Dong Li, Martin Maerz, Tobias Gerber, Gerald Deboy, Leo Lorenz.: 'Analysis and design of a 1MHz LLC Resonant Converter with Coreless transformer driver'. PCIM Conference, Shanghai. 2007
- [6] M Mao, D Tchobanov, D Li, M Maerz.: 'Design optimization of a 1MHz half bridge CLL resonant converter'. IET Power Elec

### Revision History

#### Major changes since the last revision

Page or Reference	Description of change
12, 13, 14, 15, 16	Revise schematic value, add PCB solder side legend and revise BOM typo

#### Trademarks of Infineon Technologies AG

AURIX™, C166™, CanPAK™, CIPOS™, CIPURSET™, CoolMOS™, CoolSET™, CORECONTROL™, CROSSAVE™, DAVE™, DI-POL™, EasyPIM™, EconoBRIDGE™, EconoDUAL™, EconoPIM™, EconoPACK™, EiceDRIVER™, eupec™, FCOS™, HITFET™, HybridPACK™, I<sup>2</sup>RF™, ISOFACE™, IsoPACK™, MIPAQ™, ModSTACK™, myd™, NovalithIC™, OptiMOS™, ORIGA™, POWERCODE™, PRIMARION™, PrimePACK™, PrimeSTACK™, PRO-SIL™, PROFET™, RASIC™, ReverSave™, SatRIC™, SIEGET™, SINDRION™, SIPMOS™, SmartLEWISTM, SOLID FLASH™, TEMPFET™, thinQ!™, TRENCHSTOP™, TriCore™.

#### Other Trademarks

Advance Design System™ (ADS) of Agilent Technologies, AMBA™, ARM™, MULTI-ICE™, KEIL™, PRIMECELL™, REALVIEW™, THUMB™, µVision™ of ARM Limited, UK. AUTOSAR™ is licensed by AUTOSAR development partnership. Bluetooth™ of Bluetooth SIG Inc. CAT-iq™ of DECT Forum. COLOSSUS™, FirstGPS™ of Trimble Navigation Ltd. EMV™ of EMVCO, LLC (Visa Holdings Inc.). EPCOS™ of Epcos AG. FLEXGO™ of Microsoft Corporation. FlexRay™ is licensed by FlexRay Consortium. HYPERTERMINAL™ of Hilgraeve Incorporated. IEC™ of Commission Electrotechnique Internationale. IrDAT™ of Infrared Data Association Corporation. ISO™ of INTERNATIONAL ORGANIZATION FOR STANDARDIZATION. MATLAB™ of MathWorks, Inc. MAXIM™ of Maxim Integrated Products, Inc. MICROTEC™, NUCLEUS™ of Mentor Graphics Corporation. MIPI™ of MIPI Alliance, Inc. MIPS™ of MIPS Technologies, Inc., USA. muRata™ of MURATA MANUFACTURING CO., MICROWAVE OFFICE™ (MWO) of Applied Wave Research Inc., OmniVision™ of OmniVision Technologies, Inc. Openwave™ Openwave Systems Inc. RED HAT™ Red Hat, Inc. RFMD™ RF Micro Devices, Inc. SIRIUS™ of Sirius Satellite Radio Inc. SOLARIS™ of Sun Microsystems, Inc. SPANSION™ of Spansion LLC Ltd. Symbian™ of Symbian Software Limited. TAIYO YUDEN™ of Taiyo Yuden Co. TEAKLITE™ of CEVA, Inc. TEKTRONIX™ of Tektronix Inc. TOKO™ of TOKO KABUSHIKI KAISHA TA. UNIX™ of X/Open Company Limited. VERILOG™, PALLADIUM™ of Cadence Design Systems, Inc. VLYNQ™ of Texas Instruments Incorporated. VXWORKS™, WIND RIVER™ of WIND RIVER SYSTEMS, INC. ZETEX™ of Diodes Zetex Limited.

Last Trademarks Update 2011-11-11

[www.infineon.com](http://www.infineon.com)

Edition 2015-11-06

Published by

Infineon Technologies AG  
81726 Munich, Germany

© 2015 Infineon Technologies AG.  
All Rights Reserved.

Do you have a question about any aspect of this document?

Email: [erratum@infineon.com](mailto:erratum@infineon.com)

Document reference

ANDEMO\_2015xx\_PL21\_xxx

#### Legal Disclaimer

THE INFORMATION GIVEN IN THIS APPLICATION NOTE (INCLUDING BUT NOT LIMITED TO CONTENTS OF REFERENCED WEBSITES) IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

#### Information

For further information on technology, delivery terms and conditions and prices, please contact the nearest Infineon Technologies Office ([www.infineon.com](http://www.infineon.com)).

#### Warnings

Due to technical requirements, components may contain dangerous substances. For information on the types in question, please contact the nearest Infineon Technologies Office. Infineon Technologies components may be used in life-support devices or systems only with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

**Данный компонент на территории Российской Федерации****Вы можете приобрести в компании MosChip.**

Для оперативного оформления запроса Вам необходимо перейти по данной ссылке:

<http://moschip.ru/get-element>

Вы можете разместить у нас заказ для любого Вашего проекта, будь то серийное производство или разработка единичного прибора.

В нашем ассортименте представлены ведущие мировые производители активных и пассивных электронных компонентов.

Нашей специализацией является поставка электронной компонентной базы двойного назначения, продукции таких производителей как XILINX, Intel (ex.ALTERA), Vicor, Microchip, Texas Instruments, Analog Devices, Mini-Circuits, Amphenol, Glenair.

Сотрудничество с глобальными дистрибуторами электронных компонентов, предоставляет возможность заказывать и получать с международных складов практически любой перечень компонентов в оптимальные для Вас сроки.

На всех этапах разработки и производства наши партнеры могут получить квалифицированную поддержку опытных инженеров.

Система менеджмента качества компании отвечает требованиям в соответствии с ГОСТ Р ИСО 9001, ГОСТ Р В 0015-002 и ЭС РД 009

**Офис по работе с юридическими лицами:**

105318, г.Москва, ул.Щербаковская д.3, офис 1107, 1118, ДЦ «Щербаковский»

Телефон: +7 495 668-12-70 (многоканальный)

Факс: +7 495 668-12-70 (доб.304)

E-mail: [info@moschip.ru](mailto:info@moschip.ru)

Skype отдела продаж:

moschip.ru  
moschip.ru\_4

moschip.ru\_6  
moschip.ru\_9